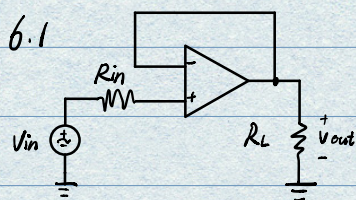


After-class assignment 3



Solution:


Since no current flows into either input terminal.

$$V^+ = V_{in}$$

Since there is no voltage difference between the two input terminal.

$$V_{out} = V^- = V^+ = V_{in}$$

Therefore $V_{out} = V_{in}$.

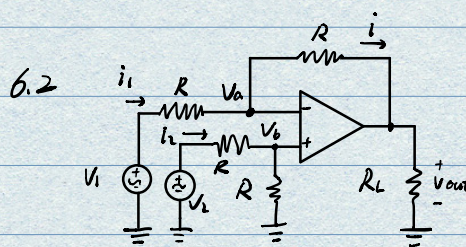

Solution:

Apply KCL to node a.

$$0 = \frac{V_1}{R} + \frac{V_{out} - V_a}{R}$$

Apply KCL to node b.

$$\frac{V_2}{R} = 0 + \frac{V_b}{R}$$

Since $V_a = V_b$

$$V_{out} = V_a - V_1$$

$$V_{out} = V_b - V_1$$

$$V_{out} = V_2 - V_1$$

7.1

(1) The current i is related to the voltage across the capacitor

$$i_1 = C \frac{dv_1}{dt} = 5 \text{ mF} \times \frac{d}{dt}(-20)$$

$$= 5 \text{ mF} \times 0$$

$$= 0 \text{ A}$$

$$(2) \quad i_2 = C \frac{dv_2}{dt} = 5 \text{ mF} \times (-10 e^{-5t})$$

$$= -50 e^{-5t} \text{ (mA)}$$

7.3

$$W_C(t) = \frac{1}{2} C V^2$$

$$= \frac{1}{2} \times 1000 \text{ nF} \times (1.5 \cos 10^5 t)^2$$

$$= 1.125 \times 10^{-3} \cos^2(10^5 t)$$

$$W|_{t=50 \mu\text{s}} = 1.125 \times 10^{-3} \cos^2(10^5 \times 50 \times 10^{-6})$$

$$= 1.125 \times 10^{-3} \cos^2(10^5 \times 5 \times 10^{-6} \times \frac{180^\circ}{\pi})$$

$$= 1.125 \times 10^{-3} (0.080666)$$

$$= 90.52 \mu\text{J}$$

Hence, the energy stored in the capacitor at $t=50 \mu\text{s}$ is $90.52 \mu\text{J}$

7.5

$$(a) \quad V = L \frac{di}{dt} = 3 \frac{di}{dt}$$

$$V_{\max} = 3 \times 10^3 \text{ V} = 3 \text{ kV}$$

$$V_{\min} = 3 \times (-10^3) \text{ V} = -3 \text{ kV}$$

$$(b) \quad V = L \frac{di}{dt} = 3 \frac{di}{dt}$$

$$V_{\max} = 3 \times \frac{1}{12 \times 10^{-6}} = 250000 \text{ V} = 250 \text{ kV}$$


$$V_{\min} = 3 \times \left(-\frac{1}{64 \times 10^{-6}}\right) = -46875 \text{ V} \approx -46.88 \text{ kV}$$

$$(c) \quad V = L \frac{di}{dt} = 3 \frac{di}{dt}$$

$$V_{\max} = 3 \times 1 = 3 \text{ V}$$

$$V_{\min} = 3 \times \left(-\frac{1}{1 \times 10^{-9}}\right) = -3 \times 10^9 \text{ V} = -3 \text{ GV}$$

7.8

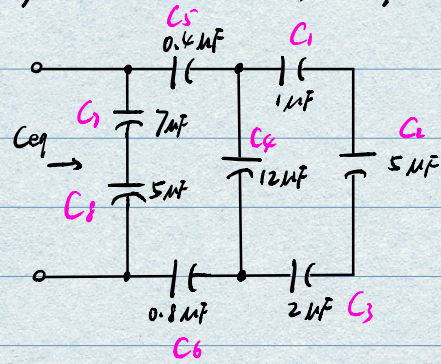


Solution:

Since capacitors C_1, C_2, C_3 are in series,

$$C_{eq1} = \frac{1}{\frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3}} = \frac{1}{\frac{1}{1} + \frac{1}{5} + \frac{1}{2}} = \frac{10}{17} \mu\text{F}$$


Rewrite the diagram.

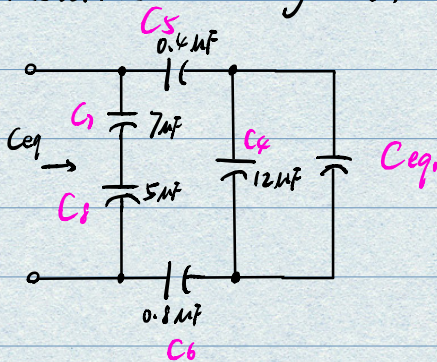

Since capacitors C_4, C_{eq1} are in parallel,

$$C_{eq2} = C_4 + C_{eq1} = \left(12 + \frac{10}{17}\right) \mu\text{F}$$

Rewrite the diagram.

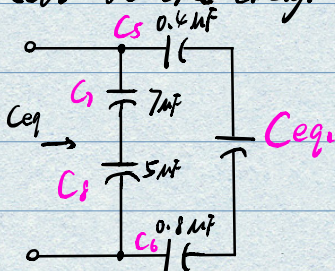


Since C_5, C_6, C_{eq2} and C_7, C_8 are in series,

$$C_{eq3} = \frac{1}{\frac{1}{C_5} + \frac{1}{C_6} + \frac{1}{C_{eq2}}} = \frac{1}{\frac{1}{0.4} + \frac{1}{0.8} + \frac{1}{12 + \frac{10}{17}}} = \frac{428}{1639} \approx 0.26 \mu\text{F}$$

$$C_{eq4} = \frac{1}{\frac{1}{C_7} + \frac{1}{C_8}} = \frac{1}{\frac{1}{7} + \frac{1}{5}} = \frac{35}{12} \approx 2.92 \mu\text{F}$$

Rewrite the diagram.

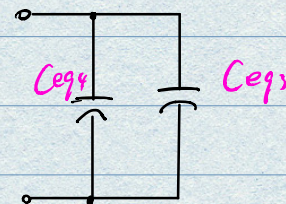

Since C_{eq3} and C_{eq4} are in parallel,

$$C_{eq} = C_{eq3} + C_{eq4} = 0.26 + 2.92 = 3.18 \mu F$$