

EEE109 Lab 2 – Transistors

Student ID numbers: 1931254

Submission date: 3/12/2020

Abstract

The objectives of the project are: Understand the physical structure and operation of the bipolar junction transistor; make a measurement of the input and output characteristics of a transistor; design and build a simple common-emitter amplifier. In the project, the approach used is based on control variable method; build the circuit; use DMM to regulate the components; measure the outcomes. From the project, we found the input characteristics are that before the voltage reaches a certain value (turn-on voltage), the current changes very little with the voltage; after it reaches a high-speed increase. The output characteristics are that before the voltage reaches a certain value (turn-on voltage), the current increases quickly; after it reaches a low speed. In the project, we fully understood the structure and features of the transistor and have the ability to build a common-emitter amplifier circuit. In conclusion, the project helps us to learn more about the input and output characteristics and common-emitter amplifier role of the transistor.

1. Background

A bipolar junction transistor is a three-terminal semiconductor device that consists of two p-n junctions which are able to amplify or magnify a signal. The three terminals of the BJT are the base (B), the collector (C), and the emitter (E) as shown in figure 1. The bipolar transistor 2N3904 we will use in this experiment is a typical NPN transistor.

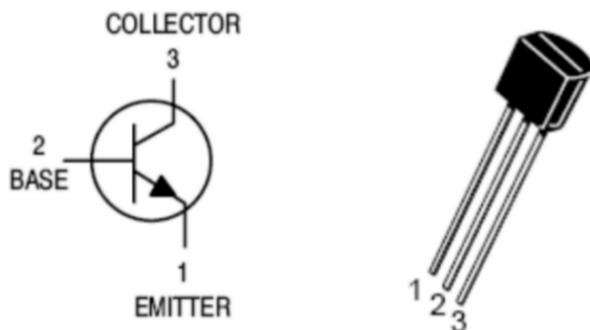


Figure 1 Bipolar junction transistor

The bipolar junction transistor is one of the most essential semiconductor device because of its three applications which are switch circuits, digital logic circuits, and amplifier circuits. When it is used to amplify current, the transistor is biased in the forward-active mode, where the collector current represents as a function of the base current. The relationship between the collector current and base current is $I_c = \beta I_B$. In this experiment, we will focus on the common-emitter configuration of BJT bias. The base of the BJT serves as the input and the collector serves as the output. The emitter of the BJT is common to both input and output.

2. Aims and Objectives

The objectives of the project are:

1. Understand the physical structure and operation of the bipolar junction transistor.

2. Make a measurement of the input and output characteristics of a transistor.
3. Design and build a simple common-emitter amplifier.

3. Experiment/Methodology

3.1 Transistor diagrams and connections

During the whole project, the first thing we should do is establishing the type of transistor we use and the names of each pin. So we used the digital multimeter to check the connections on the given transistor. We connected two of the pins by digital multimeter in a diode mode to see the values on the screen to decide which one is collector, emitter, or base.

After our measurement, we figured out the connections of the given transistor and got the correct answer of what type it is. Also, we measured the turn-on voltages for the two junctions.

3.2 Input Characteristics

In this part, we began to measure the input characteristics of the BJT.

First, we set up a circuit as shown in Figure 2 by using two d.c. power supplies and several resistors and most important bipolar transistor.

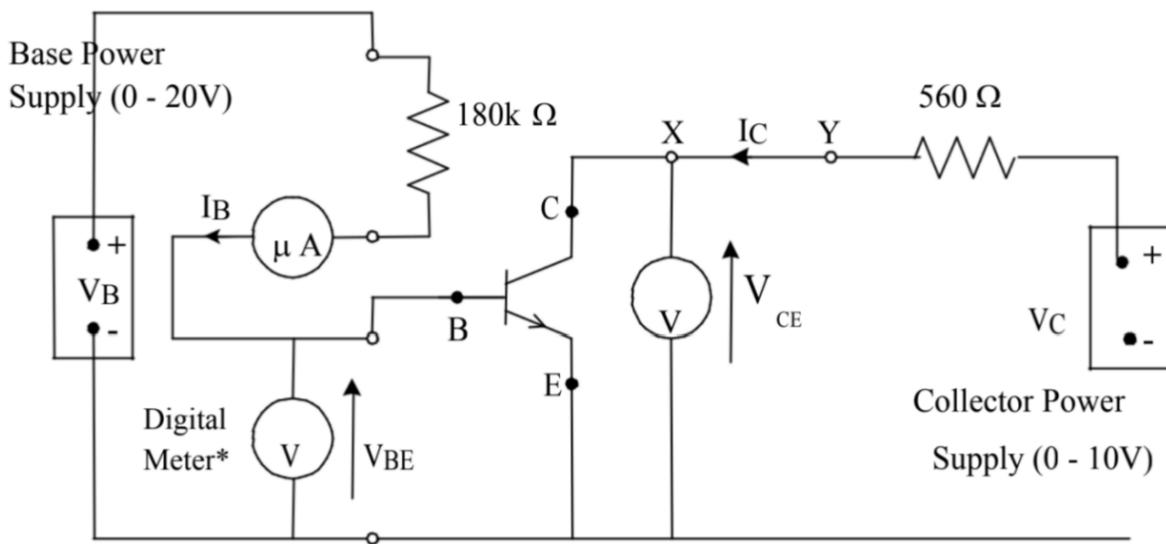


Figure 2 Circuit diagram to measure the transistor characteristics

Then we adjusted the base and collector power supply to make $V_B = 0$ and $V_{CE} = 5 \text{ V}$.

After that, we adjusted V_B to $20, 40, 70 \mu\text{A}$ by scanning the value of V_{BE} to see when it increases rapidly.

Finally, based on the values we recorded, we plotted the graph of I_B against V_{BE} as shown in figure 5.

For the part (b), we set the V_{CE} to 10 V, repeated the above operation and got another graph as shown in figure 6.

3.3 Output Characteristics

In this part, we began to measure the output characteristics of the BJT.

We used the same circuit as shown as figure 2 but changed the place of the digital ammeter to the collector to measure d.c. current. Then we measured I_C by setting V_{CE} to 0.05, 0.1, 0.2, 0.4V etc., in a doubling sequence up to 10V when $I_B = 0, 20, 40, 70\mu A$.

Finally, we plotted collector current I_C against collector-emitter voltage V_{CE} for four different base current I_B as shown in figure 7.

3.4 Common-Emitter Amplifier

In this part, we focused on the common-emitter amplifier application of the BJT.

At the beginning, we constructed the circuit as shown in figure 3.

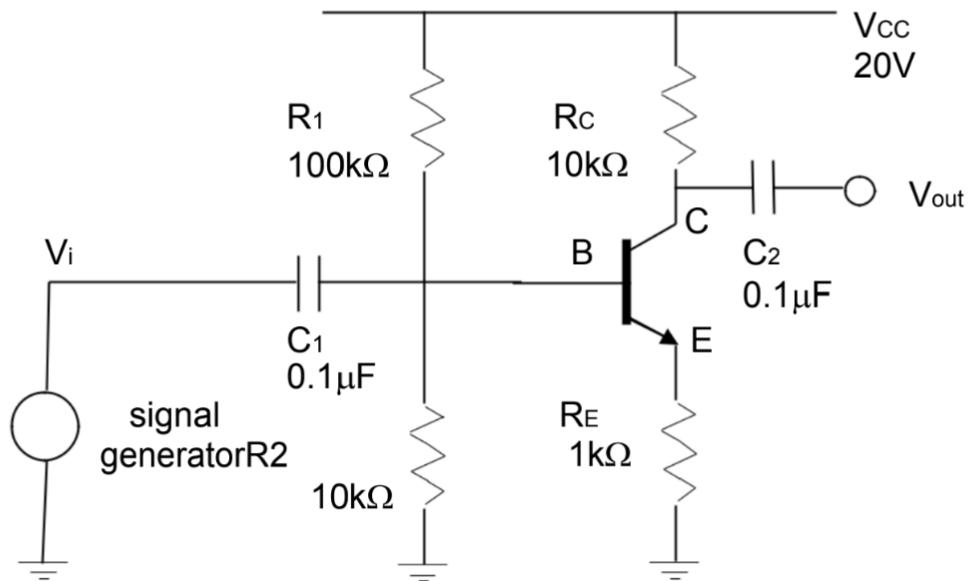


Figure 3 Common emitter amplifier using a single voltage supply

For part (a), we used an oscilloscope to monitor the input and output voltage. And then we made a rough sketch of the waveforms but using a sinusoidal V_{in} of 5 kHz and a 0.5V amplitude. At last, we compared the results with the predicted amplification by using the formula $A_v = -\frac{R_C}{R_E}$.

For part (b), we removed the a.c. input signal and used the digital multimeter to measure V_C , V_B , and V_E .

After that, we introduced an ac input signal which is 0.5V amplitude, 5 kHz. We monitored when the V_{out}

becomes clipped or distorted by increasing V_{in} 's amplitude. During the period, one of us regulated the V_{in} and the other one watched the screen on the oscilloscope to see whether the waveform begins to clipped. Finally, we recorded the input voltage when the output voltage became clipped.

4. Results

4.1 Transistor diagrams and connections

(a) The diagram of transistor is shown in figure 4.

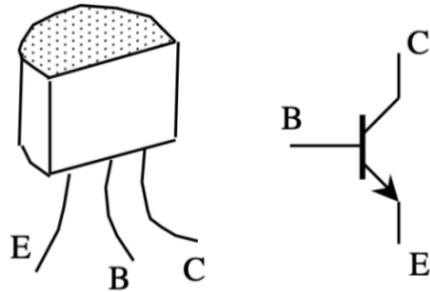


Figure 4 Bipolar junction transistor (NPN type)

The three pins of the given transistor are shown above, and the the arrow in the right part of the figure indicates the direction of emitter current.

(b) Based on the measurement of DMM, the transistor is an npn transistor. And the turn-on voltage is 0.65V. The turn-on voltage of the BJT is V_{BE} , whose value is 0.65V during the experiment.

4.2 Input Characteristics

For $V_{CE} = 5$ V, the graph of I_B against V_{BE} is shown in figure 5.

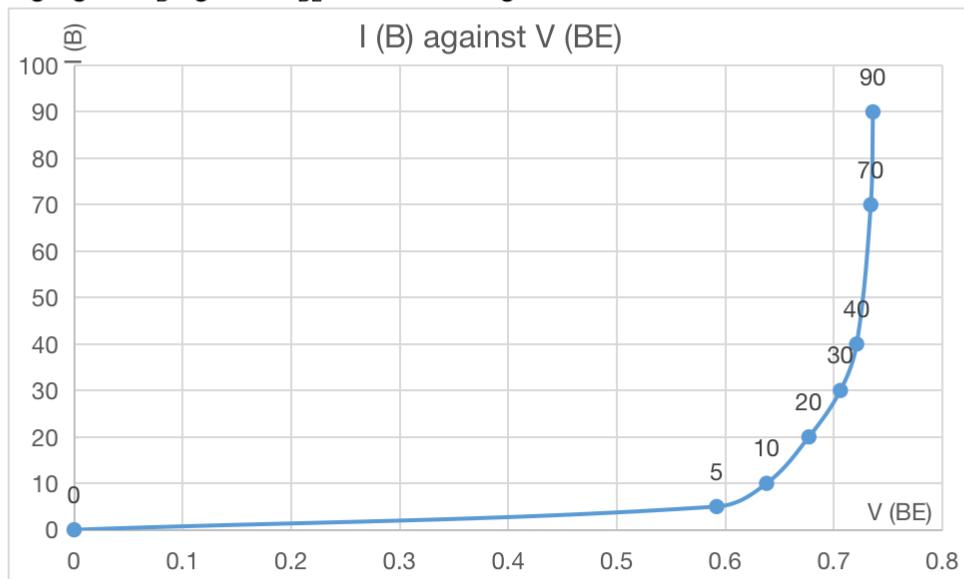
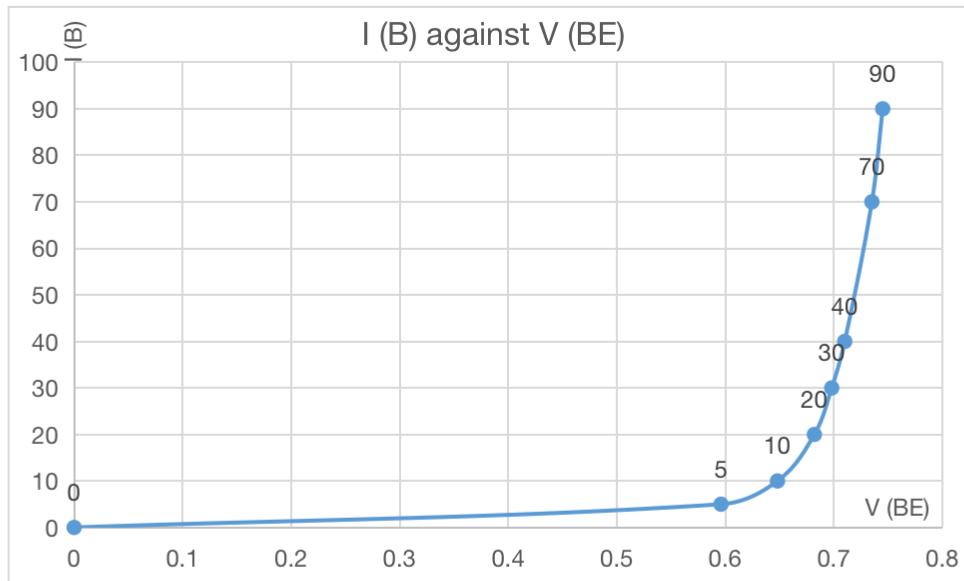


Figure 5 I_B plotted against V_{BE} ($V_{CE} = 5$ V)

The x axis represents base-emitter voltage V_{BE} (V) and the y axis represents current across base I_B (μ A).

For $V_{CE} = 10$ V, the graph of I_B against V_{BE} is shown in figure 6.

Figure 6 I_B plotted against V_{BE} ($V_{CE} = 10$ V)


The x axis represents base-emitter voltage V_{BE} (V) and the y axis represents current across base I_B (μA).

From these two graphs, we found that there is a rapid increase of I_B at around $V_{BE} = 0.65$ V and the values in graph 2 are not significantly different from those in graph 1.

This characteristic shows that before achieving the turn-on voltage, there is little current flows across the transistor, and there is no direct relationship between the turn-on voltage and the input voltage. Therefore, the two figures differ little.

4.3 Output Characteristics

The graph of I_C against V_{CE} is shown in figure 7.

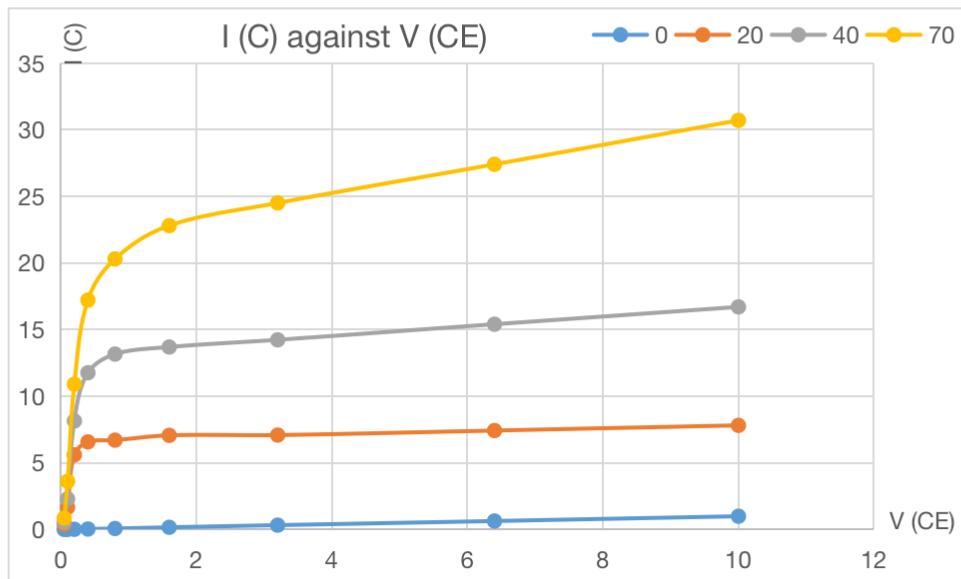Figure 7 I_C plotted against V_{CE} with different I_B


The x axis represents collector-emitter voltage V_{CE} (V) and the y axis represents current across collector I_C (μA).

For $V_{CE} < V_{BE}(\text{on})$, the B-C junction becomes forward biased, and the transistor is in the saturation mode, and the collector current increases sharply while V_{CE} increases. For $V_{CE} > V_{BE}(\text{on})$, the B-C junction is reverse biased and the transistor is in the forward-active mode. Therefore, there is a finite slope to the curves.

Since I_C equals to βI_B , the bigger the value of I_B , the bigger I_C is. Therefore, there exist four different lines on the diagram.


4.4 Common-Emitter Amplifier

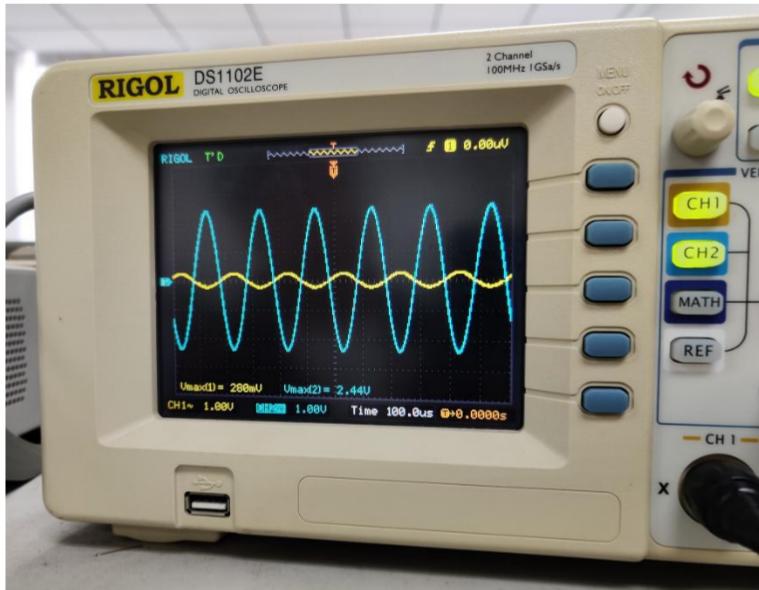(a) The input and output signals on an oscilloscope are shown as follows.



In the diagram, the amplitude of input voltage is 400mV and output voltage is 4.88V. Therefore, the amplification A_v is $- \frac{4.88}{0.4} = - 12.2$. For the predicted amplification, $A_v = - \frac{R_C}{R_E} = - \frac{10 \text{ k}\Omega}{1 \text{ k}\Omega} = - 10$. So there is little difference between the predicted value and measured value, which proves the common-emitter amplifier's typical role as an amplifier. Also, the phase agree perfectly in the diagram.

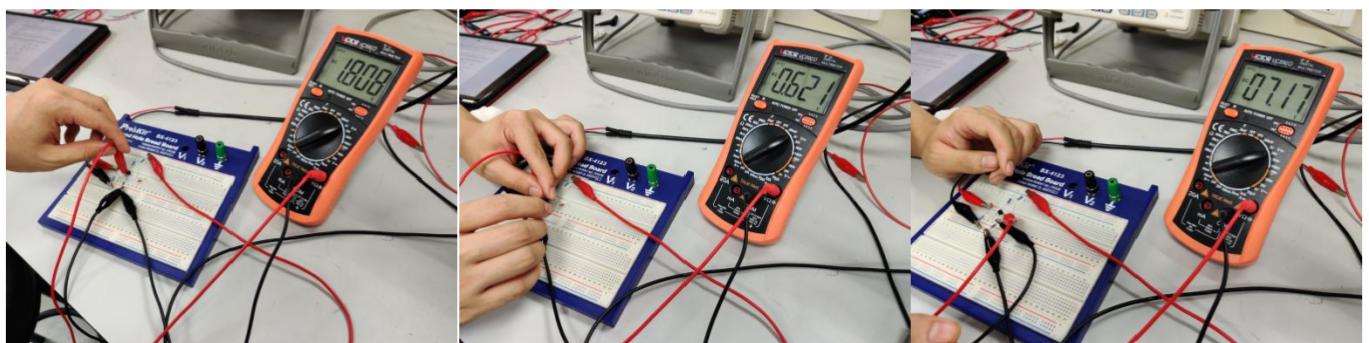(b) After removing the a.c. input signal, $V_C = 1.808 \text{ V}$, $V_B = 0.621 \text{ V}$, $V_E = 7.17 \text{ V}$.



By the simulation of LTspice as shown in figure 8, the predicted values are $V_C = 1.79 \text{ V}$, $V_B = 0.657 \text{ V}$, $V_E = 7.61 \text{ V}$.


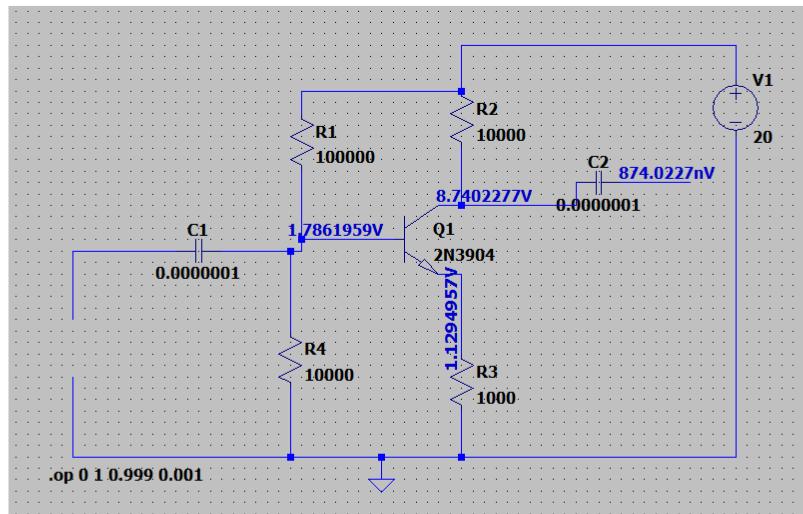


Figure 8 The simulation on the LTspice

Therefore, there is little difference between the predicted values and the measured values.

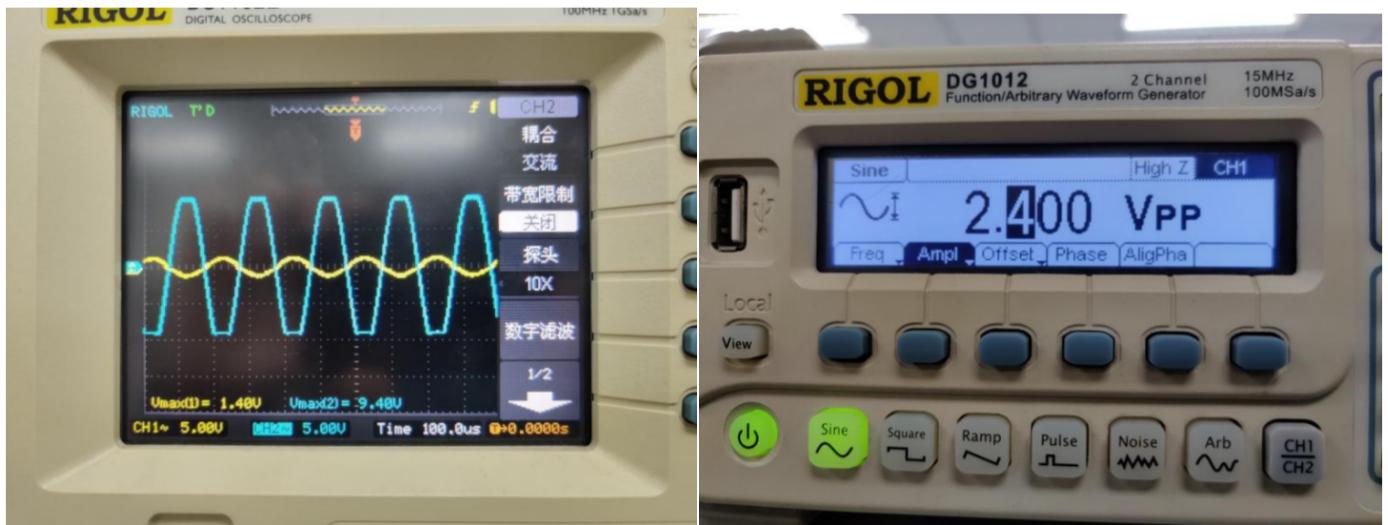After introducing the a.c. input signal again, at $V_{in} = 2.4$ V, the V_{out} becomes clipped.



At this point, the amplitude corresponds to 2.4Vpp

When $V_{in} > V_C + V_B$, the transistor turns on, and the output voltage is clipped to $V_C + V_B = 1.808 + 0.621 = 2.429$. Therefore, when $V_{in} = 2.4$ V, V_{out} becomes clipped.

5. Result Discussion

Project achievements:

1. Fully understand the physical structure and operation of the bipolar junction transistor.
2. Make a successful measurement of the input and output characteristics of a transistor.
3. Successfully design and build a simple common-emitter amplifier.

The outcome of the project is that we finally figured out the input and output characteristics and common-emitter amplifier role of the transistor, which will help students a lot in the future study, such as the use of the bipolar transistor in linear amplifier applications.

The methodology works well in this project and is applicable to other projects. First, build the circuit; second, regulate the values of components; finally, measure and record the values we need. In other projects such as the experiments on diodes, we also used this methodology, thus proving the applicability of the methodology.

6. Conclusions

In summary, a series of experiments on the transistor are conducted to find the input and output characteristics and common-emitter amplifier role of it. Moreover, the physical structure and operation of the transistor are understood.

There are some experimental errors in the experiment, the reasons we assumed are as follows:

1. Any measuring instrument has a certain accuracy level, and there will be measurement errors.
2. The actual value of any actual component will not remain unchanged, and is affected by temperature, humidity, voltage, and current. For example, the higher the carbon film resistance temperature, the lower the resistance, and the higher the metal film resistance temperature, the greater the resistance.

To improve the accuracy of the experiment, we can use more accurate electronic devices and components of the circuit. Moreover, we should measure more times to get an average value to eliminate the accidental errors.