

Assignment 1

1.

(a) Acceptor impurity atoms should be added to achieve electron concentration.

(b) At room temperature ($T = 300K$),

$$n_i = BT^{\frac{3}{2}} e^{\left(\frac{-E_g}{2kT}\right)} = (5.23 \times 10^{15})(300)^{\frac{3}{2}} e^{\left(\frac{-1.1}{2(86 \times 10^{-6})(300)}\right)} = 1.5 \times 10^{10} \text{ cm}^{-3}$$

Since donor concentration $n_o \gg n_i$,

$$p_o = \frac{n_i^2}{n_o} = \frac{(1.5 \times 10^{10})^2}{7 \times 10^{15}} \approx 3.21 \times 10^4 \text{ cm}^{-3}$$


(c) Since $p_o \leq 10^6 \text{ cm}^{-3}$, $n_i = \sqrt{n_o p_o} \leq \sqrt{7 \times 10^{15} \times 10^6} \approx 8.37 \times 10^{10} \text{ cm}^{-3}$

When n_i achieve $n_{i\max}$, T achieve T_{\max} .

$$n_{i\max} = BT_{\max}^{\frac{3}{2}} e^{\left(\frac{-E_g}{2kT_{\max}}\right)}$$

$$8.37 \times 10^{10} = (5.23 \times 10^{15}) T_{\max}^{\frac{3}{2}} e^{\left(\frac{-1.1}{2(86 \times 10^{-6}) T_{\max}}\right)}$$

$$T_{\max} = 324 \text{ K}$$

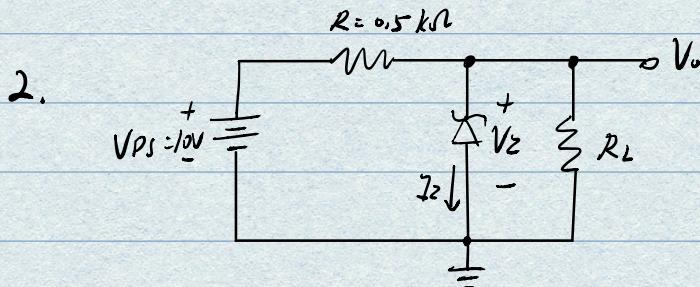

(a) When $R_L = \infty$, $V_o = V_{PS} - IR = V_o - \frac{V_{PS} - V_2}{R + R_2} \cdot R$

$$= 10 - \frac{10 - 5.6}{500 + 10} \times 500 \approx 5.686 \text{ V}$$

$$(b) V'_2 = V_2 - I_2 \times r_2 = 5.6V - 0.1 \text{ mA} \times 10 \text{ }\Omega = 5.599 \text{ V}$$

$$V_{o\max} = \frac{V_{PS\max} - V'_2}{R + r_2} r_2 + V_2 = \frac{11 - 5.599}{500 + 10} \times 10 + 5.599 \approx 5.706 \text{ V}$$


$$V_{o\min} = \frac{V_{PS\min} - V'_2}{R + r_2} r_2 + V_2 = \frac{9 - 5.599}{500 + 10} \times 10 + 5.599 \approx 5.667 \text{ V}$$

The output voltage change $\Delta V_o = V_{o\max} - V_{o\min} = 0.039 \text{ V}$

$$(c) R_{TH} = R_1 // r_2 = \frac{500 \times 10}{500 + 10} \approx 9.8 \Omega$$

$$V_{TH} = \frac{V_{DS} - V_2}{R + r_2} r_2 + V_2 = \frac{10 - 5.6}{500 + 10} \times 10 + 5.6 \approx 5.686 \text{ V}$$
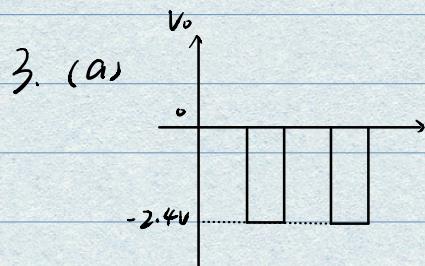
$$V_o = \frac{V_{TH}}{R_{TH} + R_L} R_L = \frac{5.686}{9.8 + 2000} \times 2000 \approx 5.658 \text{ V}$$




From the diagram, $-5 \text{ V} \leq V_2 \leq 20 \text{ V}$

when $V_2 = 20 \text{ V}$, diode is off, $V_o = 0$

when $V_2 = -5 \text{ V}$, $V_o = V_2 + V + V_r = -2.4 \text{ V}$

(b)

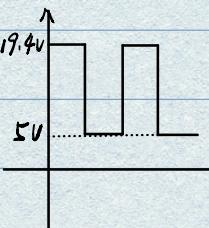

When $V_1 = 20 \text{ V}$, the diode is on.

$$V_o = V_1 - V_r = 20 - 0.6 = 19.4 \text{ V}$$

When the diode is off, $V_o = 5 \text{ V}$

4. (a) When $V_1 = V_2 = 10 \text{ V}$,

diode D_1 and D_2 are off

$$I_{D1} = I_{D2} = 0$$

$$V_o = 10 \text{ V}$$

(b) When $V_1 = 10 \text{ V}$, $V_2 = 0$,

D_1 is off and D_2 is on.

$$I_{D1} = 0, I_{D2} = \frac{10 - V_r - V_2}{0.5 + 9.5} = 0.94 \text{ mA}$$

$$V_o = 10 - I_a R = 10 - 0.94 \text{ mA} \times 9.5 \text{ k}\Omega = 1.07 \text{ V}$$

(c) When $V_1 = 10 \text{ V}$, $V_2 = 5 \text{ V}$,

D_1 is off and D_2 is on.

$$I_{D_1} = 0, \quad I_{D_2} = \frac{10 - V_r - V_s}{0.5 + 9.5} = 0.44 \text{ mA}$$

$$V_o = 10 - I_{D_2} R = 10 - 0.44 \times 9.5 = 5.82 \text{ V}$$

(d) When $V_r = 0, V_s = 0,$

D_1 and D_2 are on.

$$\text{Therefore } \frac{I}{2} = \frac{10 - V_r - 9.5}{0.5}$$

$$I = \frac{9.4}{9.75} \approx 0.964 \text{ mA}$$

$$I_{D_1} = I_{D_2} = 0.482 \text{ mA}$$

$$V_o = 10 - I R = 10 - 0.964 \times 9.5 = 0.842 \text{ V}$$

$$5. (a) V_{DS(sat)} = V_{GS} - V_{TN}$$

$$= 2.2 - 0.4 = 1.8 \text{ V}$$

$$V_{DS} = 2.2 \text{ V} > V_{DS(sat)}$$

Thus the transistor is in saturation region.

$$(b) V_{DS(sat)} = V_{GS} - V_{TH}$$

$$= 1 - 0.4 = 0.6 \text{ V}$$

$$V_{DS} = -0.6 \text{ V} < V_{DS(sat)}$$

Thus in nonsaturation region.

$$(c) V_{DS(sat)} = V_{GS} - V_{TH}$$

$$= 0 - 0.4 = -0.4 \text{ V} < 0$$

Thus in cut-off region.

$$6. V_{SD(sat)} = V_{SG} + V_{TP} = 2 - 0.5 = 1.5 \text{ V}$$

Thus in (a)(b). $V_{SD} < V_{SD(sat)}$

nonsaturation region.

in (c), (d), $V_{SD} > V_{SD(sat)}$

saturation region.

$$K_p = \frac{k_p}{2} \cdot \frac{W}{L} = \frac{50}{2} \cdot \frac{12}{0.8} = 375 \mu A/V^2 = 0.375 mA/V^2$$

Since (a), (b) in nonsaturation region.

$$\begin{aligned}(a) \quad i_D &= K_p [2(V_{SG} + V_{TP})V_{SD} - V_{SD}^2] \\ &= 0.375 \times [2(2 - 0.5) \times 0.2 - 0.2^2] \\ &= 0.21 \text{ mA}\end{aligned}$$

$$\begin{aligned}(b) \quad i_D &= K_p [2(V_{SG} + V_{TP})V_{SD} - V_{SD}^2] \\ &= 0.66 \text{ mA}\end{aligned}$$

Since (c), (d) in saturation region.

$$\begin{aligned}(c) \quad i_D &= K_p (V_{SG} + V_{TP})^2 \\ &= 0.375 \times (2 - 0.5)^2 \\ &\approx 0.84 \text{ mA}\end{aligned}$$

$$(d) \quad i_D = K_p (V_{SG} + V_{TP})^2 \approx 0.84 \text{ mA}$$

$$7. (a) \quad I_B = \frac{I_E}{1 + \beta} = \frac{1.2}{1 + 80} \approx 0.0148 \text{ mA} = 14.8 \mu \text{A}$$

$$I_C = \left(\frac{\beta}{1 + \beta}\right) I_E = \frac{80}{1 + 80} \times 1.2 \approx 1.185 \text{ mA}$$

$$\alpha = \frac{\beta}{1 + \beta} \approx 0.9877$$

$$V_C = 5 - I_C \cdot R_C = 2.63 \text{ V}$$

$$(b) \quad I_B = \frac{I_E}{1 + \beta} = \frac{0.8}{1 + 80} \approx 0.009877 \text{ mA} = 9.88 \mu \text{A}$$

$$I_C = \left(\frac{\beta}{1 + \beta}\right) I_E = \frac{80}{1 + 80} \times 0.8 \approx 0.790 \text{ mA}$$

$$\alpha = \frac{\beta}{1 + \beta} \approx 0.9877$$

$$V_C = 5 - I_C \cdot R_C = 3.42 \text{ V}$$


$$(c) I_B = \frac{I_E}{1+\beta} = \frac{1.2}{1+120} \approx 9.92 \mu A$$

$$I_C = \left(\frac{\beta}{1+\beta}\right) I_E = \frac{120}{1+120} \times 1.2 \approx 1.190 \text{ mA}$$

$$\alpha = \frac{\beta}{1+\beta} \approx 0.9917$$

$$V_C = 5 - I_C \cdot R_C = 2.62 \text{ V}$$

8. Redraw the diagram.

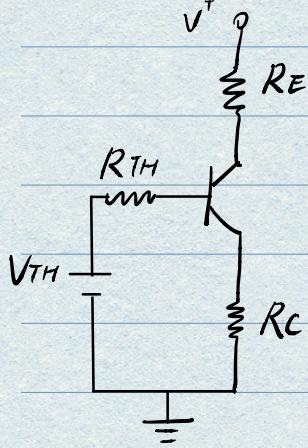

$$(a) R_{TH} = R_1 // R_2 = \frac{R_1 \times R_2}{R_1 + R_2} = \frac{40 \times 60}{40 + 60} = 20 \Omega$$

$$V_{TH} = V^+ \cdot \frac{R_2}{R_1 + R_2} = 1.25 \text{ V}$$

$$I_{BQ} = \frac{V_{TH} - V_{BE(on)}}{R_{TH} + (1+\beta)R_E} = \frac{1.25 - 0.7}{20 + (1+90) \times 0.7} \approx 6.57 \text{ mA}$$

$$I_{CQ} = \beta I_{BQ} \approx 0.591 \text{ mA}$$

$$V_{ECQ} = V^+ - V_{EB(on)} - V_C$$

$$= 2.5 - 0.7 - 0.591 \times 1.6$$

$$= 1.135 \text{ V}$$

$$(b) I_{CQ}' = \beta I_{BQ} = \beta \frac{V_{TH} - V_{BE(on)}}{R_{TH} + (1+\beta)R_E} = 120 \times \frac{1.25 - 0.7}{20 + (1+120) \times 0.7} \approx 0.657 \text{ mA}$$

$$\frac{\Delta I_{CQ}}{I_{CQ}} \times 100\% = \frac{0.657 - 0.591}{0.591} \times 100\% \approx 11.2\%$$

$$V_{ECQ}' = V^+ - V_{EB(on)} - V_C'$$

$$= 2.5 - 0.7 - 0.657 \times 1.6$$

$$= 0.986 \text{ V}$$

$$\frac{\Delta V_{ECQ}}{V_{ECQ}} \times 100\% = \frac{1.135 - 0.986}{1.135} \times 100\% \approx 13.1\%$$

Thus the percent change in I_{CQ} is 11.2%

in V_{ECQ} is 13.1%