

Lab 3 Instructions

Dr. Bing Han

Email: Bing.Han@xjtlu.edu.cn

Office: EE220

Components

- Transistor BJT 2N3904
- Resistor $R_L = 3.9 \text{ k}\Omega$
- Resistor R_c, R_e, R_1 and R_2
 - According to **calculations**
- Capacitors
 - $2 \times 1 \mu\text{F}$
 - $2 \times 47 \mu\text{F}$



Objectives



- Find β of the Transistor
- Simulate frequency response of a common emitter amplifier
- Simulate frequency response of a common collector amplifier



Find β of the Transistor




Find the Transistor

- Find the NPN transistor 2N3904

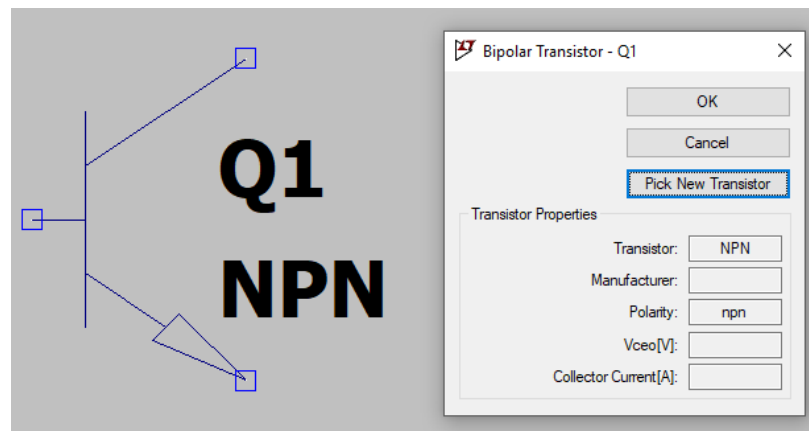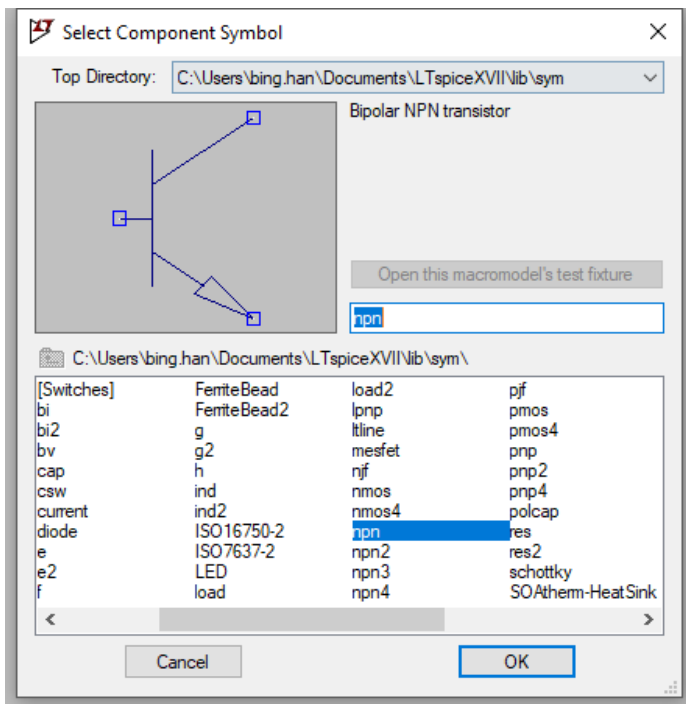


Built the Circuit

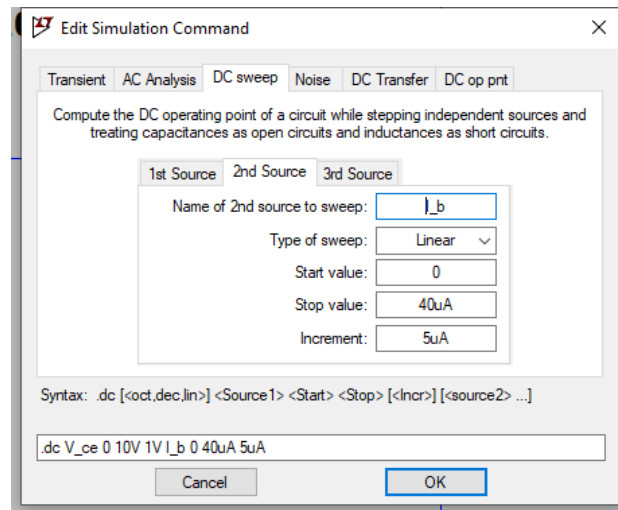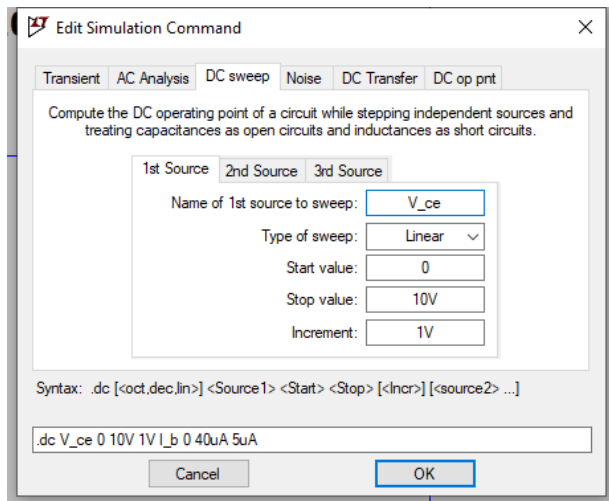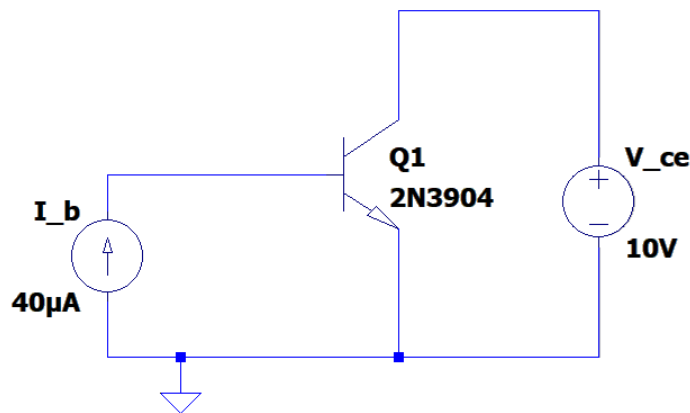- Input the circuit schematic as follows
- Pull down the “Simulate” window, select “Edit Simulation Cmd”



Find β of the Transistor

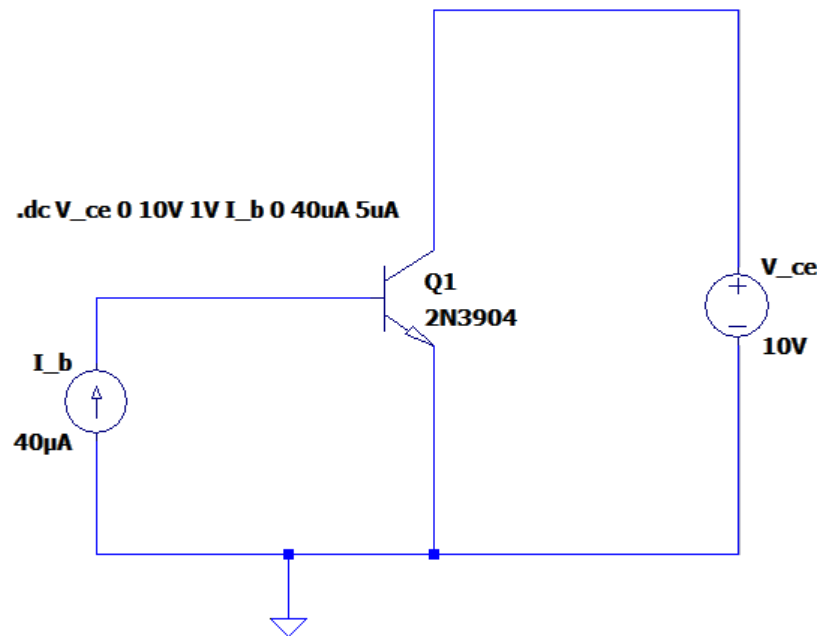
- Set the value of I_B
 - 0, 5, 10, \dots , 40 μA
- Set the value of V_{CE}
 - 0, 1, 2, \dots , 10 V
- The unit “ μA ” is represented by ‘uA’ in LTSpice
- Calculate the dc current gain β at $I_C = 5 \text{ mA}$



Common Emitter Amplifier

Common Emitter Amplifier

- Calculate the values of R_c , R_e , R_1 and R_2
 - DC Bias: $V_{CC} = 10\text{ V}$, $V_{CE} = 5\text{ V}$, $I_{CQ} = 5\text{ mA}$
- R_1 and R_2 form a **potential divider**
 - Fix the base voltage of the transistor
- $I_R = 10I_{BQ}$, $V_{BE} = 0.7\text{ V}$
- R_E helps to **stabilize the bias**
 - If the temperature increases, then extra collector current will flow.
 - If I_{CQ} increases, then I_{EQ} increases
 - V_E increases, and reducing the effective base emitter voltage and therefore stabilizing the collector current.

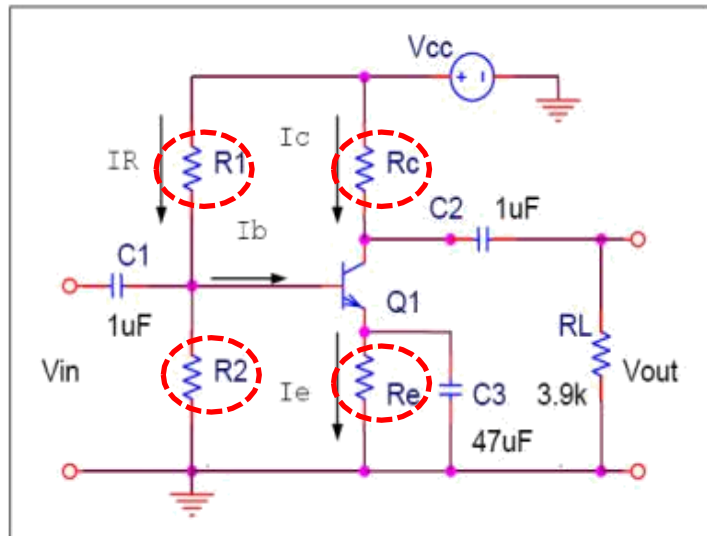

Calculations



- Assume $V_E = \frac{1}{10} V_{CC}$, $I_R = 10I_{BQ}$, $V_{CC} = 10 \text{ V}$, $V_{CE} = 5 \text{ V}$, $I_{CQ} = 5 \text{ mA}$
- Determine R_C , R_E , R_1 and R_2

$$V_{CC} = I_{CQ}R_C + V_{CE} + I_{EQ}R_E$$

$$I_{CQ} \cong I_{EQ}$$

$$V_B = V_E + 0.7$$

$$R_1 = \frac{V_{CC} - V_B}{I_R} = \frac{V_{CC} - V_B}{10I_{BQ}}$$


$$R_2 = \frac{V_B}{9I_{BQ}}$$

Common Collector Amplifier

Common Collector Amplifier



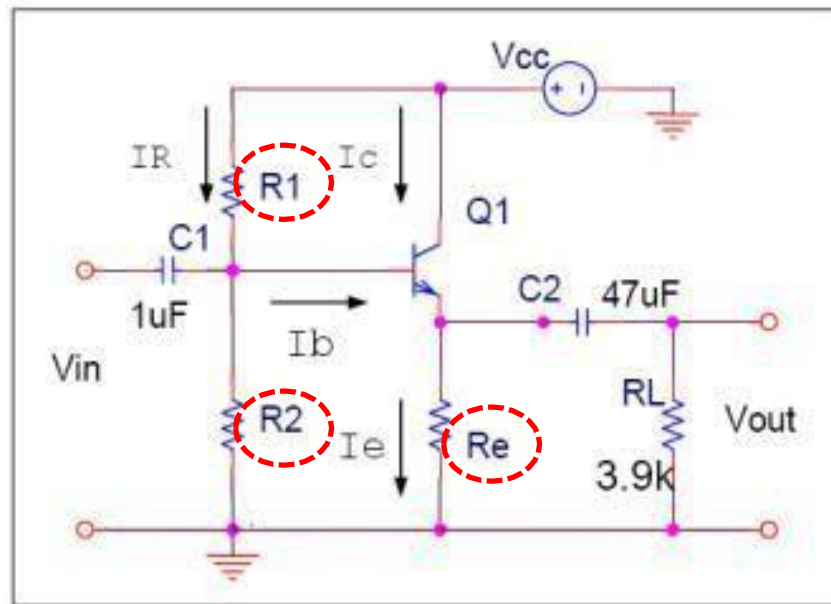- Calculate the values of R_E , R_1 and R_2
 - DC Bias: $V_{CC} = 10\text{ V}$, $V_{CE} = 5\text{ V}$, $I_C = 5\text{ mA}$
- R_1 and R_2 form a **potential divider**
 - Fix the base voltage of the transistor



Calculations



- Assume $I_R = 10I_{BQ}$, $V_{CC} = 10\text{ V}$, $V_{CE} = 5\text{ V}$, $I_{CQ} = 5\text{ mA}$
- Determine R_E , R_1 and R_2

$$V_{CC} = V_{CE} + I_{EQ}R_E$$

$$I_{CQ} \cong I_{EQ}$$

$$V_B = V_E + 0.7$$

$$R_1 = \frac{V_{CC} - V_B}{I_R} = \frac{V_{CC} - V_B}{10I_{BQ}}$$

$$R_2 = \frac{V_B}{9I_{BQ}}$$