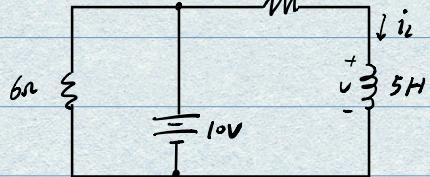


For $t \geq 0$, the circuit is



Apply KVL to the circuit.

$$-V + 4i_L + 5 \frac{di_L}{dt} = 0$$

Substituting $i_L = -\frac{V}{6}$,

$$\frac{5}{6} \frac{dv}{dt} + \left(\frac{4}{6} + 1\right)V = 0$$


$$\frac{dv}{dt} + 2V = 0$$

From the circuit, we can find that

$$V(0) = 10V$$

$$i_L = \frac{10}{4} = 2.5A$$

For $t \geq 0$, the circuit is

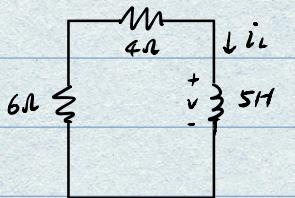

$$\text{Thus } i(t) = i_{(0)} e^{-\frac{R_{eq}t}{L}}$$


$$R_{eq} = 6 + 4 = 10\Omega$$

$$i(t) = 2.5e^{-\frac{10t}{L}}$$


$$V(t) = L \frac{di}{dt}$$

$$= 5 \frac{d}{dt}(2.5e^{-\frac{10t}{L}})$$

$$= -25e^{-\frac{10t}{L}} V$$

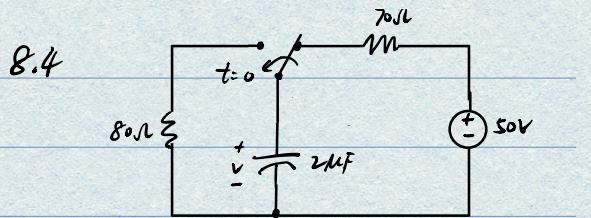

For $t \geq 0$, the circuit is

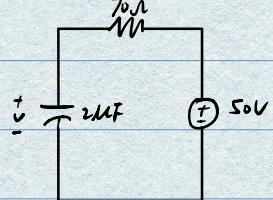


$$V(0) = 50V$$

$$T_1 = R_1 C = (8)(2 \times 10^{-6}) = 160 \times 10^{-6} s$$

$$V(t) = V(0) e^{-\frac{t}{RC}} = 50 e^{-\frac{t}{160 \times 10^{-6}}}$$

$$\text{At } t=0, V(t)=50 e^0 = 50V$$

For $t \geq 0$, the circuit is

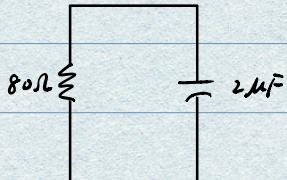

$$T_2 = R_2 C = (7)(2 \times 10^{-6}) = 140 \times 10^{-6} s$$

$$V(t) = V(0) e^{-\frac{t}{RC}} = 50 e^{-\frac{t}{140 \times 10^{-6}}}$$


$$\text{At } t=160\mu s,$$

$$V(t) = 50 e^{-\frac{160 \times 10^{-6}}{140 \times 10^{-6}}} = \frac{50}{e} \approx 18.39V$$


$$\text{Thus } V(t) = 50V \text{ when } t=0$$

$$V(t) = 18.39V \text{ when } t=160\mu s$$

8.5

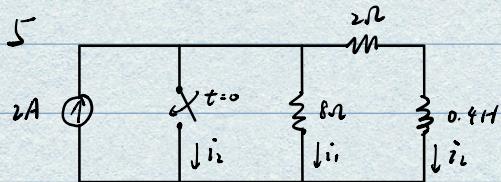


For $t < 0$, the circuit is

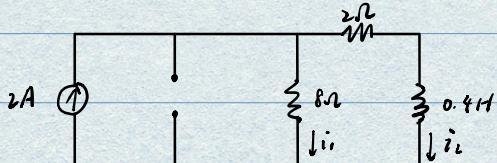

$$i_L(0^-) = 2 \times \frac{2}{8+2} = 1.6 \text{ A}$$

$$i_L(0^+) = i_C(0^-) = i_C(0) = 1.6 \text{ A}$$

For $t > 0$, the circuit is

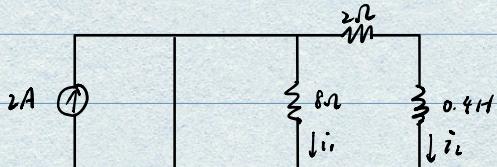

$$R_{eq} = (0||8) + 2 = 2 \Omega$$

$$\tau = \frac{L}{R_{eq}} = \frac{0.4}{2} = 0.2 \text{ s}$$

$$i_L(t) = i_L(0) e^{-\frac{t}{\tau}}$$

$$= 1.6 e^{-5t} \text{ A}$$

$$\text{when } t = 0.15, i_L = 1.6 e^{-5 \times 0.15} \approx 0.756 \text{ A}$$

$$V_{CL}(t) = L \frac{di_L(t)}{dt} = 0.4 \frac{d}{dt}(1.6e^{-5t}) \\ = -3.2e^{-5t} \text{ V}$$


$$i_1 = \frac{i_{CL} R_1 + V_{CL}(t)}{R_1} = \frac{3.2e^{-5t} - 3.2e^{-5t}}{8} = 0 \text{ A}$$

$$i_2 = 2 - i_1 - i_L = 2 - 0 - 0.756 = 1.244 \text{ A}$$


Therefore, when $t = 0.15 \text{ s}$,

$$i_L = 0.756 \text{ A}, i_1 = 0 \text{ A}, i_2 = 1.244 \text{ A}$$

8.10

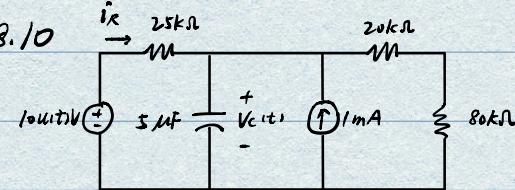

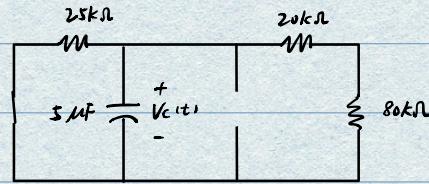Replace all the independent sources by short circuit or open circuit.



$$R_{eq} = 25 \text{ k}\Omega \parallel (20 \text{ k}\Omega + 80 \text{ k}\Omega) \\ = \frac{25 \times 10^3 \times 100 \times 10^3}{25 \times 10^3 + 100 \times 10^3} \\ = 20 \times 10^3 \Omega$$


$$\tau = R_{eq} C = 20 \times 10^3 \times 5 \times 10^{-6} \\ = 0.1 \text{ s}$$

$$\text{Since } u_{CL}(t) = \int_0^t 1 \cdot t \text{ d}t$$

$$V = 10u_{CL} \text{ V}$$

(a) for $t < 0$, the voltage source can be replaced by short circuit.

Viewing C as an open circuit.

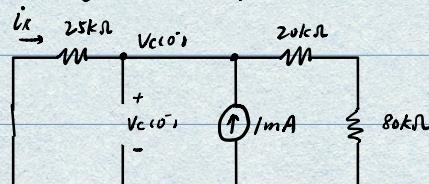

Apply KCL to node $V_{CL}(0)$.

$$\frac{V_{CL}(0)}{25 \times 10^3} + \frac{V_{CL}(0)}{20 \times 10^3 + 80 \times 10^3} = 1 \times 10^{-3}$$


$$V_{CL}(0) = 20 \text{ V}$$

(b) Since capacitor does not allow sudden changes in the voltage.

$$V_C(0^+) = V_C(0^-) = 20 \text{ V}$$

For $t > 0$, the voltage source is 10V.

(c) Viewing C as an open circuit.

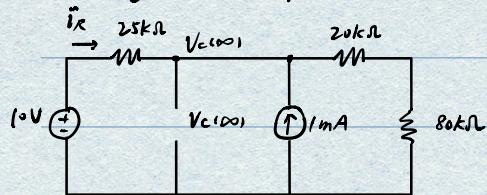

Apply KCL to node $V_C(00)$,

$$\frac{V_C(00) - 10}{25 \times 10^3} + \frac{V_C(00)}{20 \times 10^3 + 80 \times 10^3} = 1 \times 10^{-3}$$

$$V_C(00) = 28 \text{ V}$$

$$(d) V_C(t) = V_f + V_n$$

$$\begin{aligned} &= V_C(\infty) + V_n \\ &= 28 + Ae^{-\frac{t}{T}} \\ &= 28 + Ae^{-10t} \end{aligned}$$

$$\therefore V_C(0) = 28 + A = 20$$

$$\therefore A = -8$$

$$\therefore V_C(t) = 28 - 8e^{-10t}$$

$$\text{When } t = 0.08, V_C(0.08) = 28 - 8e^{-10 \times 0.08}$$

$$= 24.4 \text{ V.}$$


$$\text{Therefore, } V_C(0^+) = 20 \text{ V},$$

$$V_C(0^+) = 20 \text{ V.}$$

$$V_C(\infty) = 28 \text{ V},$$


$$V_C(0.08) = 24.4 \text{ V.}$$

8.12

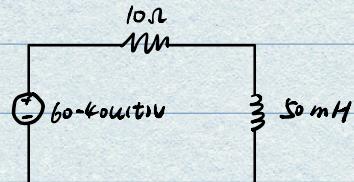

Since $u(t) = \begin{cases} 0, & t < 0 \\ 1, & t > 0 \end{cases}$

(a) For $t < 0$, the circuit is

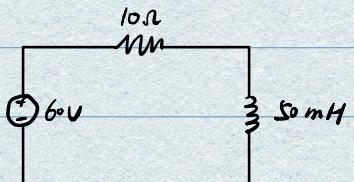


Viewing L as a short circuit,

$$V_L(0^+) = 0 \text{ V}$$

$$i_L(0^+) = \frac{60}{10} = 6 \text{ A}$$

(b) For $t > 0$, the circuit is

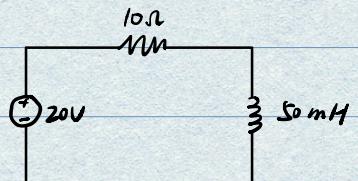

$$i_L(0^+) = i_L(0^-) = 6 \text{ A}$$

Apply KVL to the mesh.

$$V_L(0^+) = 20 - V_R$$

$$= 20 - 10 \times 6$$

$$= -40 \text{ V}$$

Therefore the magnitude of $V_L(0^+)$

is 40V.

(c) when $t \rightarrow \infty$, viewing L as a short circuit,

$$V_L(\infty) = 0 \text{ V}$$

$$i_L(\infty) = \frac{20}{10} = 2A$$

$$(d) \quad \tau = \frac{L}{R} = \frac{50 \times 10^{-3}}{10} = 5 \times 10^{-3} s$$

$$i_L(t) = i_f + i_n$$

$$= i_L(\infty) + i_n$$

$$= 2 + Ae^{-\frac{t}{\tau}}$$

$$= 2 + Ae^{-\frac{t}{5 \times 10^{-3}}}$$

$$\therefore i_L(0) = 2 + A = 6$$

$$\therefore A = 4$$

$$\therefore i_L(t) = 2 + 4e^{-\frac{t}{5 \times 10^{-3}}}$$

when $t = 3 \times 10^{-3}$,

$$i_L(3 \times 10^{-3}) = 2 + 4e^{-\frac{3}{5}} \approx 4.2A$$

Apply KVL to the mesh,

$$V_L(3 \times 10^{-3}) = 20 - 4.2 \times 10 = -22V$$

Therefore the magnitude of V_L is
22V.

So when $t = 0^-$, $|i_L| = 6A$, $|V_L| = 0V$

$t = 0^+$, $|i_L| = 6A$, $|V_L| = 40V$

$t = \infty$, $|i_L| = 2A$, $|V_L| = 0V$.

$t = 3ms$, $|i_L| = 4.2A$, $|V_L| = 22V$.

10.2

$$40 \cos(100t - 40^\circ) - 20 \sin(100t + 170^\circ)$$

$$= 40 \cos 100t \cos 40^\circ + 40 \sin 100t \sin 40^\circ -$$

$$20 \sin 100t \cos 170^\circ - 20 \cos 100t \sin 170^\circ$$

$$= (40 \cos 40^\circ - 20 \sin 170^\circ) \cos 100t +$$

$$(40 \sin 170^\circ - 20 \cos 170^\circ) \sin 100t$$

$$\approx 27.2 \cos 100t + 45.2 \sin 100t$$

$$= A \cos 100t + B \sin 100t$$

$$\text{Therefore } A = 27.2, B = 45.2$$

$$A \cos 100t + B \sin 100t$$

$$= \sqrt{A^2 + B^2} \left(\frac{A}{\sqrt{A^2 + B^2}} \cos 100t + \frac{B}{\sqrt{A^2 + B^2}} \sin 100t \right)$$

$$= \sqrt{A^2 + B^2} (\cos \theta \cos 100t + \sin \theta \sin 100t)$$

$$= \sqrt{A^2 + B^2} \cos(100t - \theta)$$

$$= \sqrt{A^2 + B^2} \cos[100t - \tan^{-1}(\frac{B}{A})]$$

$$= \sqrt{27.2^2 + 45.2^2} \cos[100t - \tan^{-1}(\frac{45.2}{27.2})]$$

$$\approx 52.9 \cos(100t - 59.1^\circ)$$

$$= C \cos(100t + \phi)$$

$$\text{Therefore } C = 52.9, \phi = -59.1^\circ$$

10.4

(a) By using polar to rectangular form transformation.

$$2 \angle 30^\circ = 2(\cos 30^\circ + j \sin 30^\circ)$$

$$= 2\left(\frac{\sqrt{3}}{2} + j\frac{1}{2}\right)$$

$$= \sqrt{3} + j \approx 1.732 + j$$

$$5 \angle -110^\circ = 5(\cos(-110^\circ) + j \sin(-110^\circ))$$

$$\approx -1.7101 - j4.698$$

$$\text{Therefore, } [(2 \angle 30^\circ) \times (5 \angle -110^\circ)](1+j2)$$

$$= (1.732 + j)(-1.7101 - j4.698)(1+j2)$$

$$= (1.7358 - j9.847)(1+j2) \quad (d)$$

$$\approx 21.4 - j6.38$$

$$(c) \frac{2-j7}{3-j} = \frac{2-j7}{3-j} \times \frac{3+j}{3+j}$$
$$= \frac{(2-j7)(3+j)}{3^2 - j^2}$$
$$= \frac{6 - j21 + j2 - 3j^2}{3^2 - j^2}$$
$$= 1.3 - j1.9$$

Convert the rectangular form into polar form $r \angle \theta$.

$$1.3 - j1.9$$

$$= \sqrt{1.3^2 + (-1.9)^2} \angle \tan^{-1}\left(\frac{-1.9}{1.3}\right)$$

$$\approx 2.30 \angle -55.6^\circ$$

$$\frac{5 \angle 80^\circ}{2 \angle 20^\circ} = \frac{5}{2} \angle 80^\circ - 20^\circ$$

$$= 2.5 \angle 60^\circ$$

$$= 2.5 (\cos 60^\circ + j \sin 60^\circ)$$

(b) By using polar to rectangular form transformation.

$$5 \angle -200^\circ = 5(\cos(-200^\circ) + j \sin(-200^\circ))$$

$$\approx -4.6985 + j1.7101$$

$$4 \angle 20^\circ = 4(\cos 20^\circ + j \sin 20^\circ)$$

$$\approx 3.7588 + j1.3681$$

$$\text{Therefore } 5 \angle -200^\circ + 4 \angle 20^\circ$$

$$= -4.6985 + j1.7101 + 3.7588 + j1.3681$$

$$\approx -0.940 + j3.08$$

$$\approx 1.25 + j2.165$$

$$8 - j4 + \left(\frac{5 \angle 80^\circ}{2 \angle 20^\circ}\right)$$

$$= 8 - j4 + 1.25 + j2.165$$

$$= 9.25 - j1.835$$

Convert the rectangular form into polar form $r \angle \theta$.

$$9.25 - j1.835$$

$$= \sqrt{9.25^2 + (-1.835)^2} \angle \tan^{-1}\left(\frac{-1.835}{9.25}\right)$$

$$\approx 9.43 \angle -11.22^\circ$$

10.7

$$(a) -5 \sin(580t - 110^\circ)$$

$$= 5 \cos(580t - 20^\circ)$$

$$I = 5 \angle -20^\circ$$

$$(b) 3 \cos 600t - 5 \sin(600t + 110^\circ)$$

$$= 3 \cos 600t - 5 \cos(600t + 20^\circ)$$

$$I = 3 \angle 0^\circ - 5 \angle 20^\circ$$

$$5 \angle 20^\circ = 5 \cos 20^\circ + j \sin 20^\circ$$

$$\approx 4.698 + j1.7101$$

$$3 \angle 0^\circ - 5 \angle 20^\circ = -1.6985 - j1.7101$$

Convert the rectangular form into

$$(c) 8 \cos(4t - 30^\circ) + 4 \sin(4t - 10^\circ)$$

$$= 8 \cos(4t - 30^\circ) - 4 \cos(4t - 10^\circ)$$

$$= 8 \angle -30^\circ - 4 \angle -10^\circ$$

$$8 \angle -30^\circ = 8[\cos(-30^\circ) + j \sin(-30^\circ)]$$

$$\approx 6.9282 - j4$$

$$4 \angle -10^\circ = 4[\cos(-10^\circ) + j \sin(-10^\circ)]$$

$$\approx 3.9392 - j0.6946$$

$$8 \angle -30^\circ - 4 \angle -10^\circ$$

$$= 2.989 - j3.3054$$

Convert the rectangular form into

polar form $r \angle \theta$.

polar form $r \angle \theta$.

$$-1.6985 - j1.7101$$

$$= \sqrt{(-1.6985)^2 + (-1.7101)^2} \angle \left[\tan^{-1}\left(\frac{-1.7101}{-1.6985}\right) + 180^\circ \right]$$

$$= 2.41 \angle (45.2^\circ + 180^\circ)$$

$$= 2.41 \angle 225.2^\circ$$


$$= 2.41 \angle (225.2^\circ - 360^\circ)$$

$$= 2.41 \angle -134.8^\circ$$

$$2.989 - j3.3054$$

$$= \sqrt{2.989^2 + (-3.3054)^2} \angle \tan^{-1}\left(\frac{-3.3054}{2.989}\right)$$

$$\approx 4.46 \angle -47.9^\circ$$

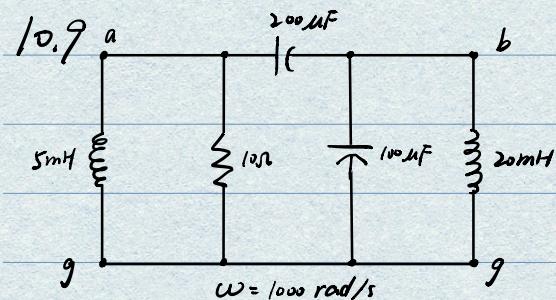

Since $\omega = 1000 \text{ rad/s}$,


$$Z_{200\mu\text{F}} = \frac{1}{j\omega C} = j \times \frac{1}{1000 \times 200 \times 10^{-6}} = -j5\Omega$$

$$Z_{5\text{mH}} = j\omega L = j \times 1000 \times 5 \times 10^{-3} = j5\Omega$$

$$Z_{100\mu\text{F}} = \frac{1}{j\omega C} = j \times \frac{1}{1000 \times 100 \times 10^{-6}} = -j10\Omega$$


$$Z_{20\text{mH}} = j\omega L = j \times 1000 \times 20 \times 10^{-3} = j20\Omega$$

Thus the equivalent circuit is

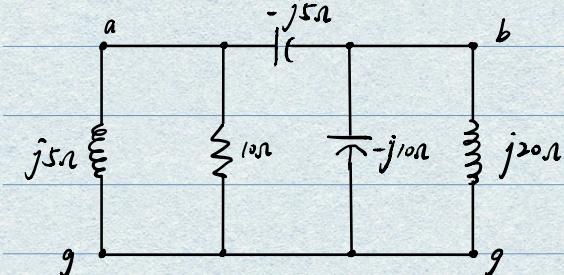

(a) For input impedance across a and g terminal.

Rewrite the circuit diagram.

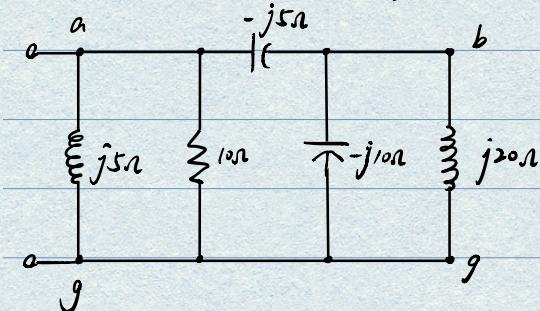

Since $j20\Omega$ is in parallel with $-j20\Omega$,

$$\begin{aligned} Z_1 &= j20\Omega \parallel -j10\Omega \\ &= \frac{j20 \cdot (-j10)}{j20 - (-j10)} = -j20\Omega \end{aligned}$$

Since Z_1 is in series with

$$-j5\Omega$$

$$Z_2 = -j20\Omega - j5\Omega = -j25\Omega$$

Since Z_2 , 10Ω , $j5\Omega$ are in parallel,

$$Z_{in} = -j25\Omega \parallel 10\Omega \parallel j5\Omega$$


$$= (18.6207 - j3.4683) \parallel j5\Omega$$

$$= \frac{17.241 + j43.103}{8.6207 + j1.552}$$

$$\approx 2.81 + j4.49 \Omega$$

(b) For input impedance across b and g terminal.

Rewrite the circuit diagram.

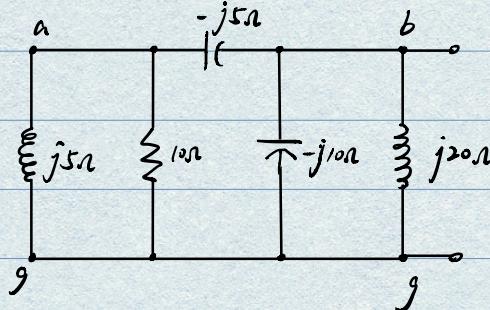

Since $j5\Omega$ is in parallel with 10Ω ,

$$\begin{aligned} Z_3 &= j5\Omega \parallel 10\Omega = \frac{10 \times j5}{10 + j5} \\ &= 2 + j4 \Omega \end{aligned}$$

Since Z_3 is in series with $-j5\Omega$.

$$Z_4 = 2 + j4 - j5 = 2 - j1\Omega$$

Since Z_4 , $-j10\Omega$, $j20\Omega$ are in parallel.

$$Z_{in} = 2 - j1\Omega \parallel -j10\Omega \parallel j20\Omega$$

$$= (1.6 - j1.2) \parallel j20\Omega$$

$$= \frac{24 + j31}{1.6 + j18.8} \approx 1.798 - j1.125 \Omega$$


$$Z_{in} = (Z_5 - Z_6) \parallel -j5\Omega$$

$$= 2 - j16\Omega \parallel -j5\Omega$$

$$= \frac{-80 - j10}{2 - j21}$$


$$\approx 0.1124 - j3.82 \Omega$$

10.13

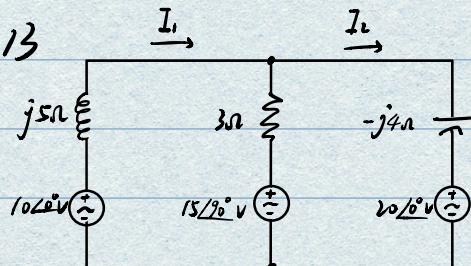

(c) For input impedance across
a and b terminal.

Rewrite the circuit diagram.

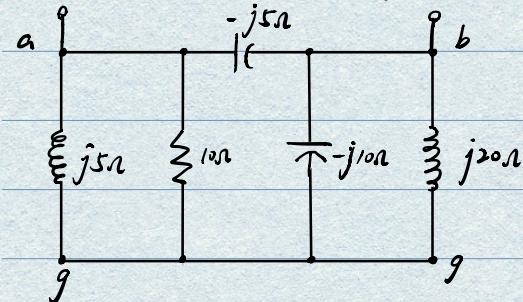

Apply KVL to mesh 1.

$$-10\angle 20^\circ + j5I_1 + 3(I_1 - I_2) + 15\angle 90^\circ = 0$$

$$-10 + (3 + j5)I_1 - 3I_2 + j15 = 0$$

$$(3 + j5)I_1 - 3I_2 = 10 - j15 \quad \text{--- (1)}$$

Apply KVL to mesh 2.

Since $j5\Omega$ is in parallel with 1Ω .

$$Z_5 = j5\Omega \parallel 1\Omega$$

$$= 2 + j4\Omega$$

$$-15\angle 90^\circ + 3(I_2 - I_1) - j4I_2 + 20\angle 0^\circ = 0$$

$$-j15 - 3I_1 + (3 - j4)I_2 + 20 = 0$$

$$-3I_1 + (3 - j4)I_2 = -20 + j15 \quad \text{--- (2)}$$

By (1) $\times \frac{3 - j4}{-90 - j40} + (2)$,

$$I_1 = \frac{3 - j4}{20 + j3}$$

$$= \frac{98.488 \angle -156.04^\circ}{20.224 \angle 8.531^\circ}$$

$$= 4.87 \angle -164.6^\circ \text{ A}$$

$$I_2 = \frac{-105 - j100}{20 + j3}$$

$$= \frac{145 \angle -136.4^\circ}{20.224 \angle 8.531^\circ}$$

$$= 7.17 \angle -144.9^\circ \text{ A}$$

Rewrite the circuit diagram.

