
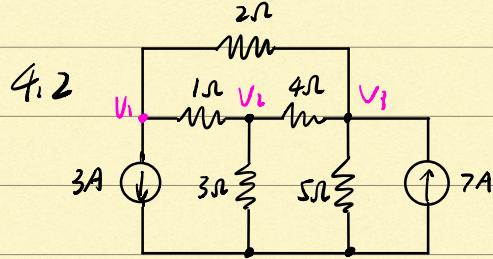


## After-class Assignment 2

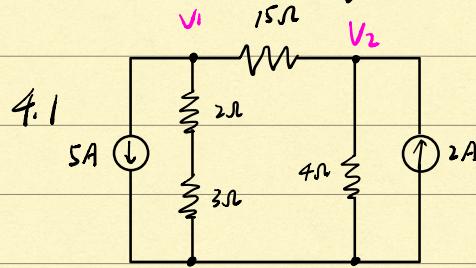

Apply KCL to node 1.

$$-5 = \frac{V_1}{2+3} + \frac{V_1 - V_2}{15}$$

$$-75 = 3V_1 + V_1 - V_2$$

$$-75 = 4V_1 - V_2 \quad \text{--- ①}$$

Apply KCL to node 1.

$$-3 = \frac{V_1 - V_2}{1} + \frac{V_1 - V_3}{2}$$

$$-6 = 2V_1 - 2V_2 + V_1 - V_3$$

$$-6 = 3V_1 - 2V_2 - V_3 \quad \text{--- ②}$$

Apply KCL to node 2.

$$2 = \frac{V_2}{4} + \frac{V_2 - V_1}{15}$$

$$120 = 15V_2 + 4V_2 - 4V_1$$

$$120 = 19V_2 - 4V_1 \quad \text{--- ③}$$

Apply KCL to node 2.

$$\frac{V_2}{3} + \frac{V_2 - V_1}{1} + \frac{V_2 - V_3}{4} = 0$$

$$4V_2 + 12V_2 - 12V_1 + 3V_2 - 3V_3 = 0$$

$$0 = -12V_1 + 19V_2 - 3V_3$$

Solve the equations.

$$\textcircled{1} + \textcircled{2} \Rightarrow 45 = 18V_2$$

$$V_2 = \frac{5}{2} V$$

$$V_1 = -\frac{145}{8} V$$

Apply KCL to node 3.

$$7 = \frac{V_3}{5} + \frac{V_3 - V_2}{4} + \frac{V_3 - V_1}{2}$$

$$140 = 4V_3 + 5V_3 - 5V_2 + 10V_3 - 10V_1$$



$$140 = -10V_1 - 5V_2 + 19V_3 \quad \text{--- ④}$$

Thus  $V_1$  is  $\frac{5}{2} V$  and  $V_2$  is  $-\frac{145}{8} V$ . Combine ①②③, solve the equations.


$$\begin{cases} -6 = 3V_1 - 2V_2 - V_3 \\ 0 = -12V_1 + 19V_2 - 3V_3 \end{cases} \Rightarrow \begin{cases} V_1 = 5.235 V \\ V_2 = 5.1175 V \\ V_3 = 11.47 V \end{cases}$$

Thus,  $V_{3A}$  is  $5.235 V$  and

$V_{7A}$  is  $11.47 V$ .

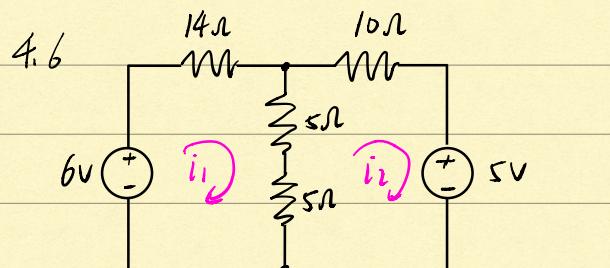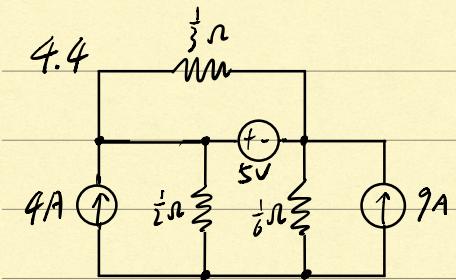

Redraw the circuit diagram.

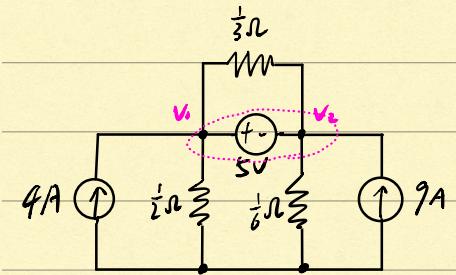

Apply KVL to mesh 1.

$$-6 + 14i_1 + (5 + 5 \times i_1 - i_2) = 0$$

$$24i_1 - 10i_2 = 6 \quad \text{--- (1)}$$

Apply KVL to mesh 2.

$$(5 + 5)(i_2 - i_1) + 10i_2 + 5 = 0$$

$$-10i_1 + 20i_2 = -5 \quad \text{--- (2)}$$

Apply KCL to 1-2 supernode.

$$4 + 9 = \frac{V_1}{\frac{1}{2}} + \frac{V_2}{\frac{1}{6}}$$

$$2V_1 + 6V_2 = 13 \quad \text{--- (1)}$$

Since there is a 5V voltage

between nodes 1 and 2,

$$V_1 - V_2 = 5 \quad \text{--- (2)}$$

Solve both equations.

$$\text{--- (1)} \times 2 + \text{--- (2)}, \text{ we get}$$

$$38i_1 = 7$$

$$i_1 = \frac{7}{38} \approx 0.1842A = 184.2mA$$

$$i_2 = -\frac{3}{19} \approx -0.1579A = -157.9mA$$


Thus  $i_1$  is 184.2mA

Combine (1) and (2), solve the equations.

and  $i_2$  is -157.9mA.

$$\begin{cases} 2V_1 + 6V_2 = 13 \\ V_1 - V_2 = 5 \end{cases} \Rightarrow \begin{cases} V_1 = 5.375V \\ V_2 = 0.375V \end{cases}$$

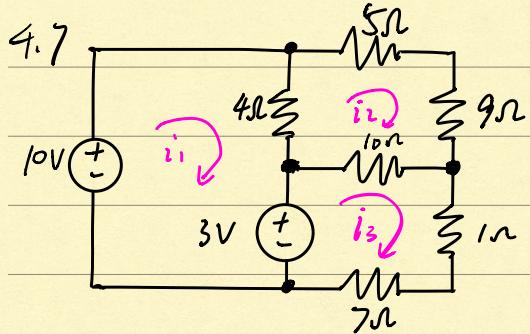Thus  $V_{4A}$  is 5.375V and  $V_{9A}$  is 0.375V.



The three mesh are assigned as indicated in the diagram.

Apply KVL to mesh 1.

$$-10 + 4(i_1 - i_2) + 3 = 0$$

$$4i_1 - 4i_2 = 7 \quad \text{--- (1)}$$

Apply KVL to mesh 2,

$$5i_2 + 9i_2 + 10(i_2 - i_3) + 4(i_2 - i_1) = 0$$

$$-4i_1 + 28i_2 - 10i_3 = 0$$

$$-2i_1 + 14i_2 - 5i_3 = 0 \quad \text{--- (2)}$$

Apply KVL to mesh 3,



$$i_3 + 7i_3 - 3 + 10(i_3 - i_2)$$

$$-10i_2 + 18i_3 = 3 \quad \text{--- (3)}$$

Combine (1), (2), (3), solve the equations.


$$\begin{cases} 4i_1 - 4i_2 = 7 \\ -2i_1 + 14i_2 - 5i_3 = 0 \\ -10i_2 + 18i_3 = 3 \end{cases} \Rightarrow \begin{cases} i_1 \approx 2.220 \\ i_2 \approx 0.470 \\ i_3 \approx 0.428 \end{cases}$$

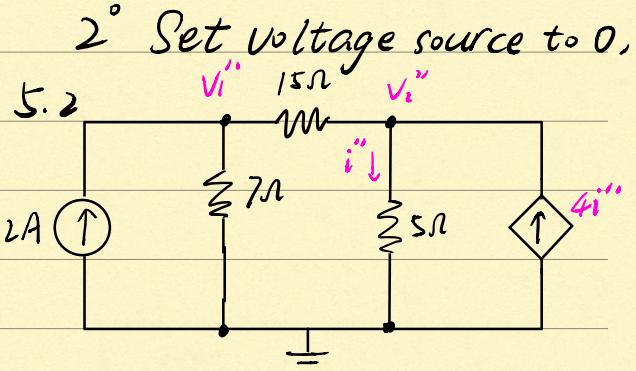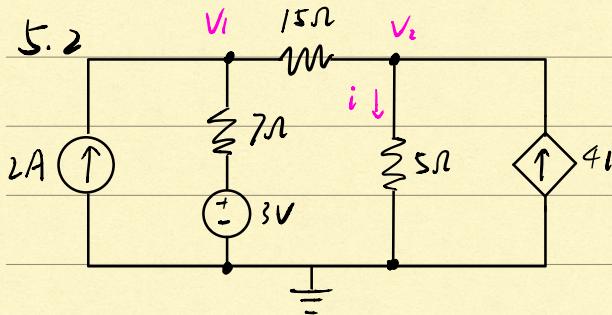Thus  $i_1$  is 2.220A and  $i_2$  is 470.0mA.



Apply superposition.

1° Set current source to 0,

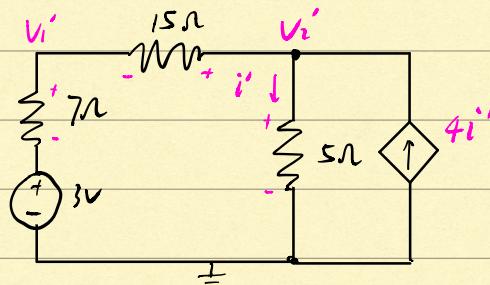

Apply KCL to node 1,

$$4i'' = i' + \frac{V_1' - V_2'}{15\Omega} \quad \text{--- (1)}$$

Thus the current on left

part of the circuit is  $3i'$ .

Apply KVL to the left mesh.

$$-3 + (7+15)(-3i') + 5i' = 0$$

$$i' = -\frac{3}{61} \quad \text{--- (2)}$$

At the middle circuit,  $\frac{V_2'}{5} = i' \quad \text{--- (3)}$

$$\text{Combine (2) (3), } V_2' = -\frac{15}{61} \approx 0.246 \text{ V} \quad \text{--- (4)}$$

$$\text{Combine (1) (2) (4), } V_1' = \frac{120}{61} \approx 1.967 \text{ V}$$

Apply KCL to node 2,

$$-2 + \frac{V_1'' - V_2''}{15} + \frac{V_1''}{7} = 0 \quad \text{--- (5)}$$

Apply KCL to node 2,

$$-4i'' + i'' + \frac{V_1'' - V_2''}{15} = 0 \quad \text{--- (6)}$$

$$\text{From 1° we have, } \frac{V_1''}{5} = i'' \quad \text{--- (7)}$$

Combine (5) (6) (7), solve the equation,

$$\left\{ \begin{array}{l} i'' = -\frac{14}{61} \approx 0.230 \text{ A} \\ V_1'' = \frac{560}{61} \approx 9.180 \text{ V} \end{array} \right.$$

$$V_2'' = -\frac{70}{61} \approx -1.148 \text{ V}$$

$$\text{Thus } V_1 = V_1' + V_1''$$







$$= 1.967 + 9.180$$

$$= 11.147 \text{ V}$$

$$V_2 = V_2' + V_2''$$

$$= 0.246 - 1.148$$

$$= -1.384 \text{ V}$$

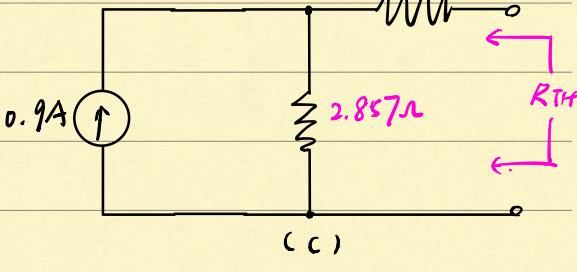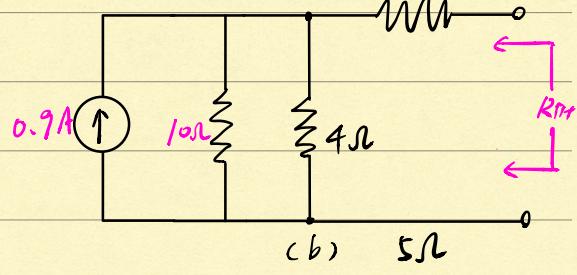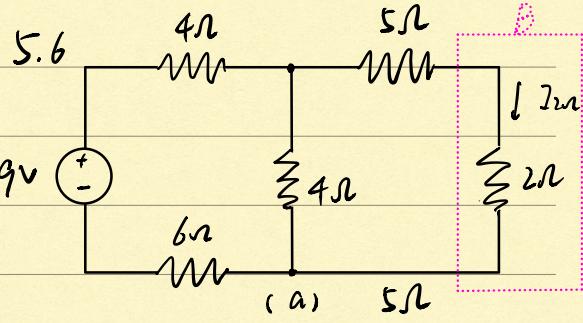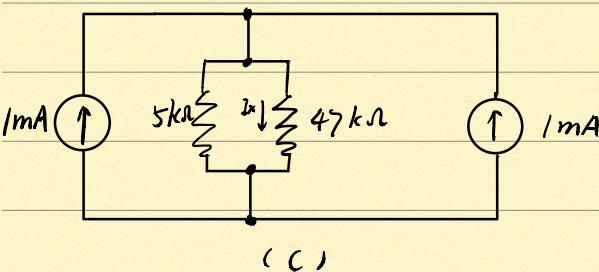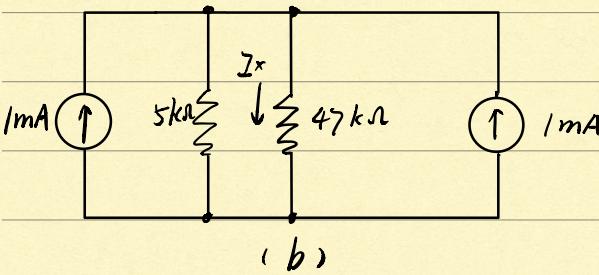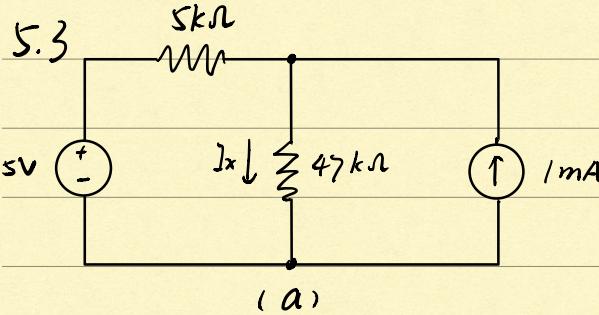

For diagram (a). Transforming voltage source to current source, as shown as diagram (b) the current is  $\frac{5V}{5k\Omega} = 1mA$ . Redrawing the circuit diagram.

Apply the current diversion.

$$Ix = (1mA + 1mA) \times \frac{5}{47+5}$$

$$= \frac{10}{52}$$

$$\approx 0.192 \text{ mA}$$


$$= 192 \mu\text{A}$$

Thus  $Ix$  is  $192 \mu\text{A}$ .

Designate the  $2\Omega$  resistor as  $B$ . For diagram (a). Transforming voltage source to current source, as shown as diagram (b)  $I = \frac{9}{10} = 0.9 \text{ A}$

Then redraw the diagram, two resistors can be drawn as (c)
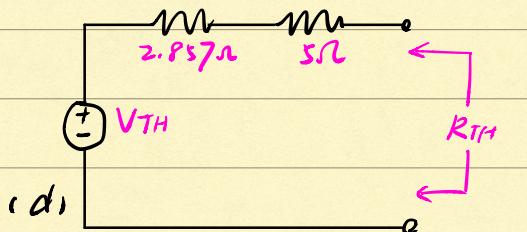
$$R_{Th} = \frac{10 \times 4}{10 + 4} \approx 2.857 \Omega$$







For diagram (c). Transforming current source to voltage source, as shown as diagram (d)

$$V_{TH} = 2.857 \times 0.9 \approx 2.571 \text{ V}$$

$$R_{TH} = 2.857 + 5 = 7.857 \text{ k}\Omega$$

$$I_{2\Omega} = \frac{V_{TH}}{R_{TH}+2} = \frac{2.571}{7.857+2} \approx 0.2608 \text{ A} = 260.8 \text{ mA}$$

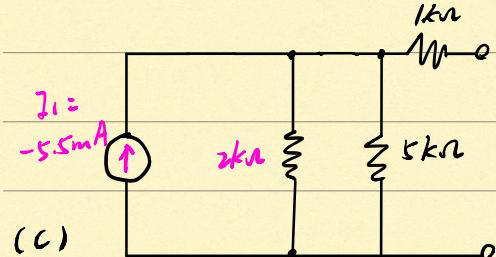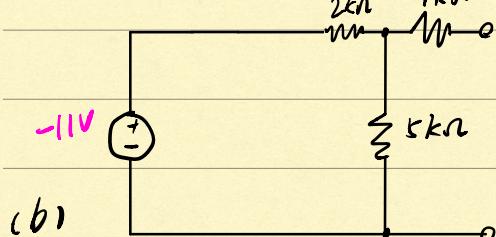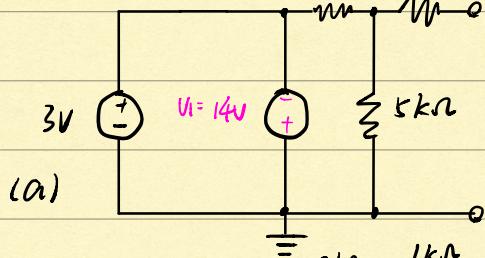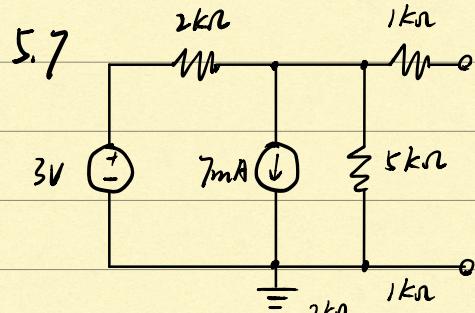Thus the current through  $2\Omega$  is  $260.8 \text{ mA}$ .



Apply the transformation on  $7\text{mA}$  current source by replacing it with a voltage source  $V_1$ , as shown in diagram (a)

$$V_1 = 2\text{k}\Omega \times 7\text{mA} = 14 \text{ V}$$

$$V_{total} = 3 + (-14) = -11 \text{ V}$$


Redraw the diagram as (b)

Apply the transformation on  $-11 \text{ V}$  voltage source by replacing it with a current source  $I_1$  and a  $2\text{k}\Omega$  resistor in diagram (c)

$$I_1 = \frac{-11 \text{ V}}{2\text{k}\Omega} = -5.5 \text{ mA}$$

$$\text{Therefore, } R_{eq} = \frac{2 \times 5}{2+5} = \frac{10}{7} \text{ k}\Omega$$

Apply the transformation on

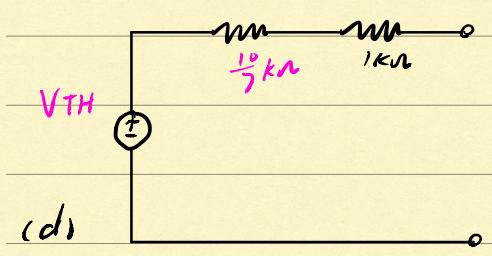

current source  $I_1$  and  $\frac{10}{7} \text{ k}\Omega$  resistor by replacing them with a voltage source  $V_{TH}$  and  $\frac{10}{7} \text{ k}\Omega$  resistor in series in diagram (d).


$$\text{Therefore. } V_{TH} = \frac{10}{7} \text{ k}\Omega \times (-5.5) \text{ mA} \approx -7.857 \text{ V}$$

$$R_{TH} = \frac{10}{7} + 1 \approx 2.429 \text{ k}\Omega$$



$$I_{TH} = \frac{V_{TH}}{R_{TH}} = \frac{-7.857 \text{ V}}{2.429 \text{ k}\Omega} \approx -3.235 \text{ mA}$$

Thus the  $V_{TH}$  is  $-7.857 \text{ V}$ ,  $R_{TH}$  is  $2.429 \text{ k}\Omega$ ,  $I_{TH}$  is  $-3.235 \text{ mA}$ .

5.11

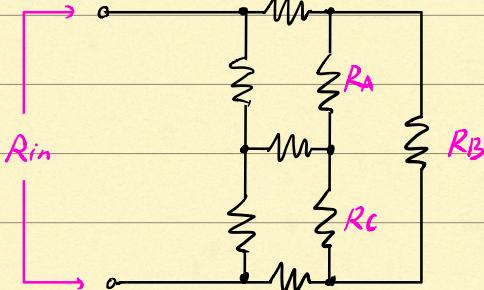

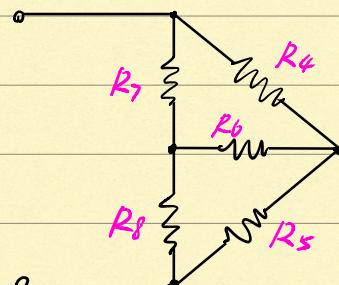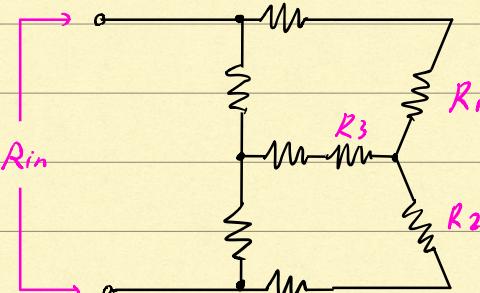
Apply  $\Delta-Y$  conversion, convert  $RA, RB, RC$  into  $R_1, R_2, R_3$ .



$$R_1 = R_2 = R_3 = \frac{10 \times 10}{10 + 10 + 10} = \frac{10}{3} \text{ }\Omega$$

$$\text{Therefore } R_4 = R_5 = R_6 = 10 + \frac{10}{3} = \frac{40}{3} \text{ }\Omega$$

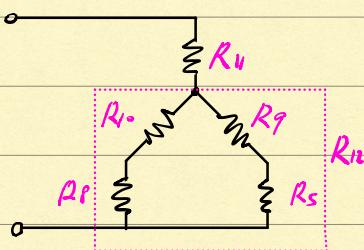Apply  $\Delta-Y$  conversion, convert  $R_4, R_6, R_7$  into  $R_9, R_{10}, R_{11}$ .



$$R_9 = \frac{R_4 R_6}{R_4 + R_6 + R_7} = \frac{\frac{40}{3} \times \frac{40}{3}}{\frac{40}{3} + \frac{40}{3} + 10} = \frac{160}{33} \Omega$$

$$R_{10} = R_{11} = \frac{\frac{40}{3} \times 10}{\frac{40}{3} + \frac{40}{3} + 10} = \frac{40}{11}$$

$$R_{12} = \frac{(R_8 + R_{10})(R_9 + R_5)}{R_8 + R_{10} + R_9 + R_5} = \frac{(10 + \frac{40}{11})(\frac{160}{33} + \frac{40}{3})}{10 + \frac{40}{11} + \frac{160}{33} + \frac{40}{3}}$$

$$R_{eq} = R_{12} + R_{11} = \frac{600}{77} + \frac{40}{11} = \frac{80}{7} \approx 11.43 \Omega$$

Thus Thévenin equivalent resistance is  $11.43 \Omega$ .