

EEE109 Assignment 2 Chapter 4, 6, 7 and 8

1. The parameters of the MOSFET in the circuit shown in Figure 1 are $V_{TN} = 0.8\text{ V}$, $K_n = 0.85\text{ mA/V}^2$, and $\lambda = 0.02\text{ V}^{-1}$

(a) Determine R_S and R_D such that $I_{DQ} = 0.1\text{ mA}$ and $V_{DSQ} = 5.5\text{ V}$

(b) Find the small-signal transistor parameters.

(c) Determine the small-signal voltage gain.

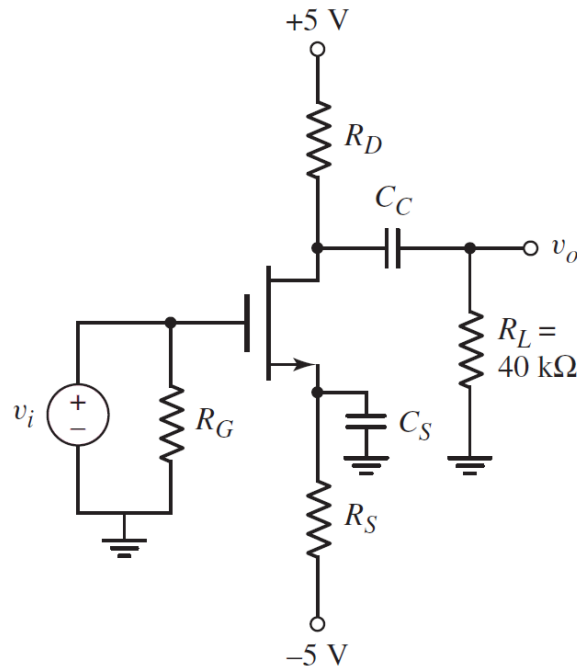


Figure 1

2. Consider the circuit show in Figure 2. The transistor parameters are $\beta = 100$ and $V_A = 100$ V.

(a) Determine R_i

(b) Determine the small-signal voltage gain A_v

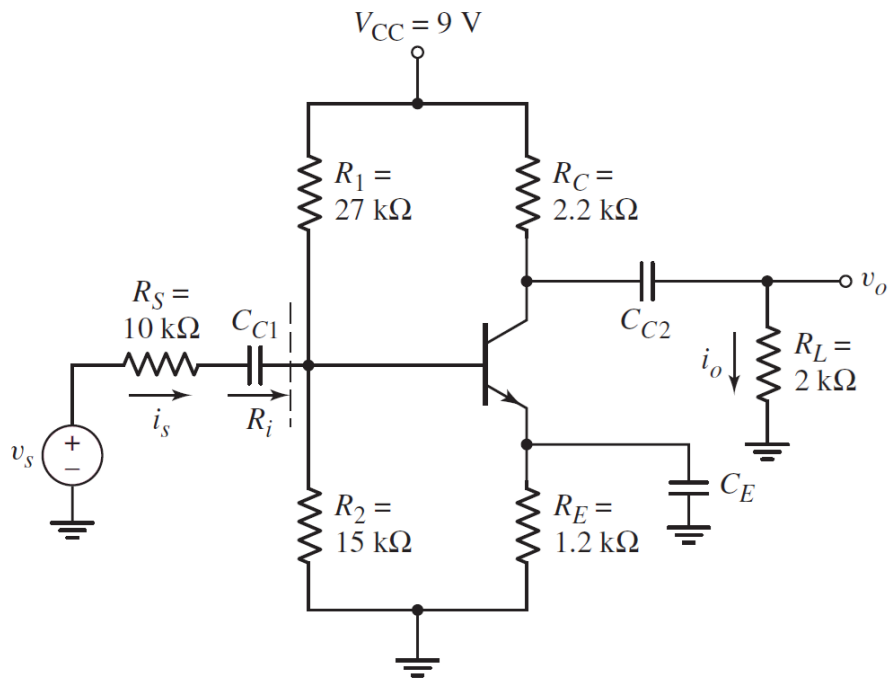


Figure 2


3. For the circuit in Figure 3, the transistor parameters are $\beta = 120$, $V_{BE}(\text{on}) = 0.7 \text{ V}$, and $V_A = 50 \text{ V}$. Let $R_{TH} = 0.1(1 + \beta)R_E$.

(a) Design a bias-stable circuit such that $I_{EQ} = 1.5 \text{ mA}$

(b) Using the results of part (a), find the small-signal mid-band voltage gain

(c) Determine the output resistance R_o

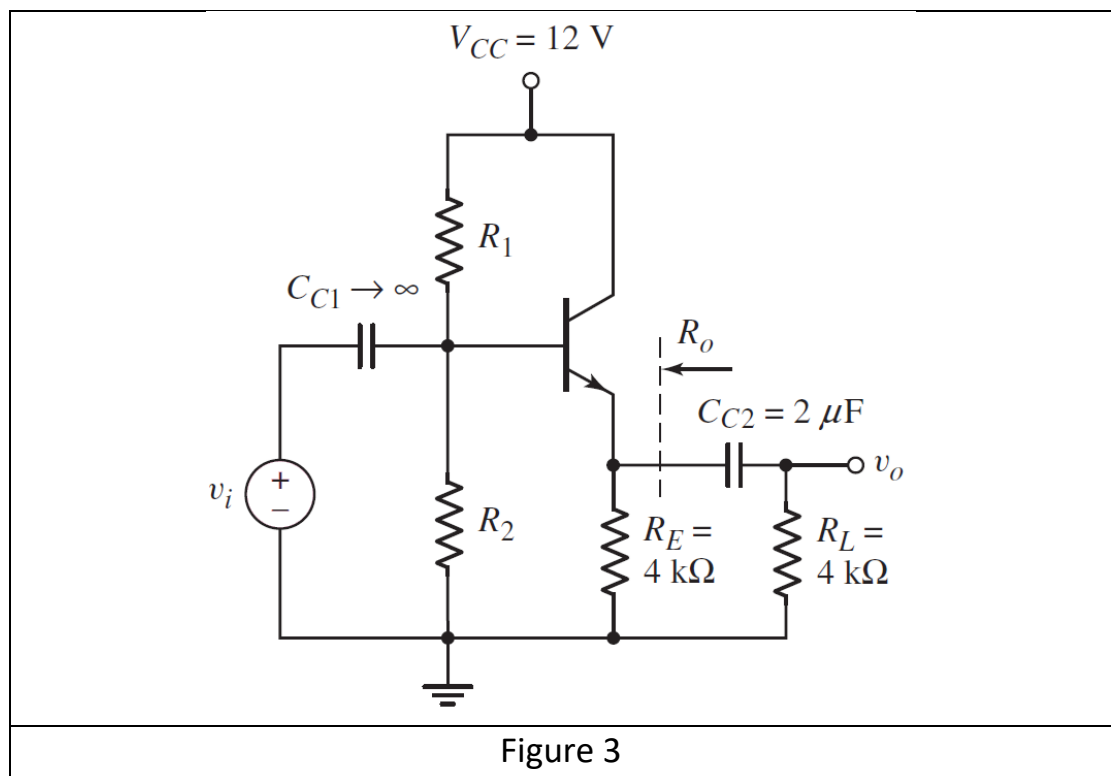(d) What is the lower 3 dB corner frequency?



4. The common-emitter circuit in Figure 4 is biased at $V_{CC} = 24\text{ V}$. The maximum transistor power is rated at $P_{Q,\max} = 25\text{ W}$. The other parameters of the transistor are $\beta = 60$ and $V_{BE}(\text{on}) = 0.7\text{ V}$.

Determine R_L and R_B such that the transistor is biased at the maximum power point.

