



2020/21 Semester 1 - Assignment(Final)

Bachelor Degree - Year 2

Electrical Circuit 1


Time Allowed : 7 Days

Student ID	Name
1931254	Zhongnan Li

Examiner's Use Only

The table below is for the record of each question score and the total mark.

Question	Mark
1	
2	
3	
Total Mark	

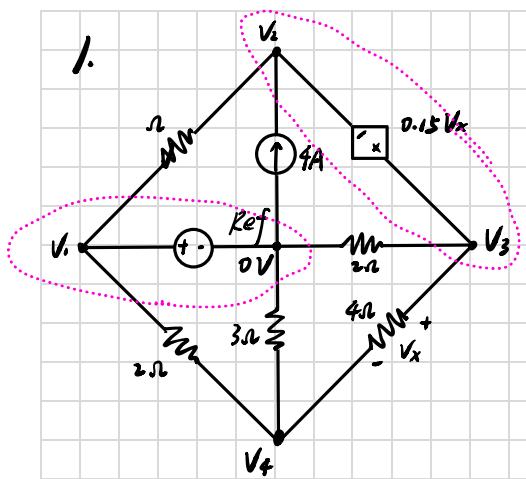

(a) Apply KCL to 3-4 supernode,

$$\frac{V_1 - V_2}{1} + 4 + \frac{-V_3}{2} + \frac{V_4 - V_3}{4} = 0$$

$$-4V_1 + 4V_2 + 3V_3 - V_4 = 16 \quad \dots \dots \textcircled{1}$$

Since there is a voltage source between node 2 and node 3.

$$V_3 - V_2 = 0.15V_x$$

$$\text{Moreover, } V_x = V_3 - V_4$$

$$\text{Therefore, } V_3 - V_2 = 0.15(V_3 - V_4)$$

$$-V_2 + 0.85V_3 + 0.15V_4 = 0 \quad \dots \dots \textcircled{2}$$

Apply KCL to 1-Ref supernode,

$$\frac{V_2 - V_1}{1} + \frac{V_4 - V_1}{2} + \frac{V_3}{2} - 4 = 0$$

$$-9V_1 + 6V_2 + 3V_3 + 5V_4 = 24 \quad \dots \dots \textcircled{3}$$

Apply KCL to node 4,

$$\frac{V_1 - V_4}{2} + \frac{V_3 - V_4}{4} + \frac{-V_4}{3} = 0$$

$$6V_1 + 3V_3 - 13V_4 = 0 \quad \dots \dots \textcircled{4}$$

Combine $\textcircled{1}$ $\textcircled{2}$ $\textcircled{3}$ $\textcircled{4}$, we have

$$\begin{cases} -4V_1 + 4V_2 + 3V_3 - 4V_4 = 16 \\ -9V_1 + 6V_2 + 3V_3 + 5V_4 = 24 \\ 6V_1 + 3V_3 - 13V_4 = 0 \\ -V_2 + 0.85V_3 + 0.15V_4 = 0 \end{cases} \quad \#$$

These four equations are the required equations.

$$(b) \begin{cases} -4V_1 + 4V_2 + 3V_3 - 4V_4 = 16 \\ -9V_1 + 6V_2 + 3V_3 + 5V_4 = 24 \\ 6V_1 + 3V_3 - 13V_4 = 0 \\ -V_2 + 0.85V_3 + 0.15V_4 = 0 \end{cases}$$

For the simultaneous equations, applying matrix inversion.

We have $\begin{bmatrix} -4 & 4 & 3 & -4 & 16 \\ -9 & 6 & 3 & 5 & 24 \\ 6 & 0 & 3 & -13 & 0 \\ 0 & -1 & 0.85 & 0.15 & 0 \end{bmatrix}$

Solve the matrix, the results are:

$$\begin{cases} V_1 = \frac{205}{126}V_4 - \frac{20}{21} \\ V_2 = \frac{269}{252}V_4 + \frac{34}{21} \\ V_3 = \frac{68}{63}V_4 + \frac{40}{21} \end{cases}$$


Since there are infinite possible values for V_4 ,
there are infinite solutions to the simultaneous equations.

If we add an additional condition $V_1 = 3V$.

the solution will be

$$V_1 = 3V, V_2 = 4.212V, V_3 = 4.527V, V_4 = 2.429V$$

#

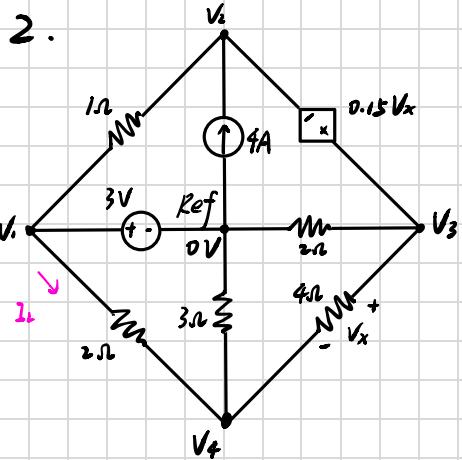


Since the circuit is the same as the circuit in Question 1, and $V_1 = 3V$, the values of voltage is solved as

$$V_2 = 4.212V, V_3 = 4.527V, V_4 = 2.429V.$$

Therefore, the current through the load resistor is
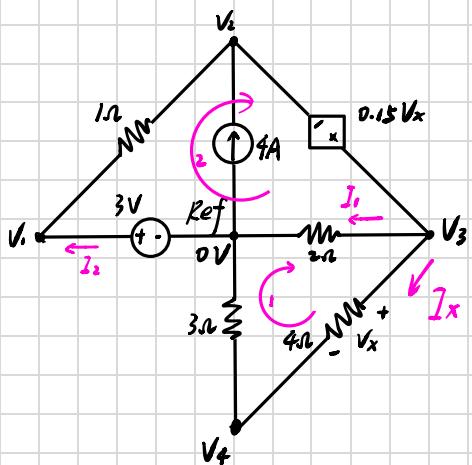
$$I_L = \frac{V_1 - V_4}{2} = \frac{3 - 2.429}{2} = 0.2855A$$



Rewrite the circuit by removing the load resistor to obtain Thevenin-equivalent-voltage.

From the circuit, the current through 4Ω resistor is $I_x = \frac{V_x}{4} A$

Apply KVL to mesh 1 made of V_4 , Ref. and V_3 .

$$\frac{V_x}{4} \cdot (3 + 4) - 2I_1 = 0$$

$$I_1 = \frac{7}{8}V_x \quad \dots\dots \textcircled{1}$$

Apply KCL to node Ref.

$$I_1 + \frac{V_x}{4} = 4 + I_2$$

$$I_2 = \frac{9}{8}V_x - 4 \quad \dots\dots \textcircled{2}$$

Apply KVL to mesh 2 made of V_1 , V_2 , V_3 , Ref.

$$2I_1 - 3 + I_2 - 0.15V_x = 0 \quad \dots\dots \textcircled{3}$$

Combine \textcircled{1}, \textcircled{2}, \textcircled{3}.

$$2 \times \frac{7}{8}V_x - 3 + \frac{9}{8}V_x - 4 - 0.15V_x = 0$$

$$V_x \approx 2.569V$$

Apply KVL to mesh made of V_1 , V_4 , and Ref.

$$3 - V_{TH} - 3 \cdot \frac{V_4}{4} = 0$$


$$3 - V_{TH} - 3 \cdot \frac{2.569}{4} = 0$$

$$V_{TH} \approx 1.073 \text{ V}$$


Therefore, Thevenin-equivalent-resistor is

$$R_{eq} = \frac{V_{TH}}{I_L} - 2 = \frac{1.073}{0.2855} - 2 \approx 1.76 \Omega$$

Thus, the Thevenin-equivalent-circuit is

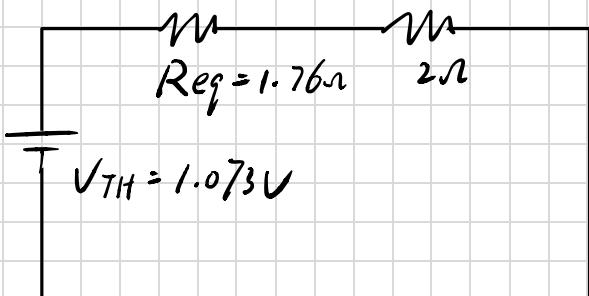

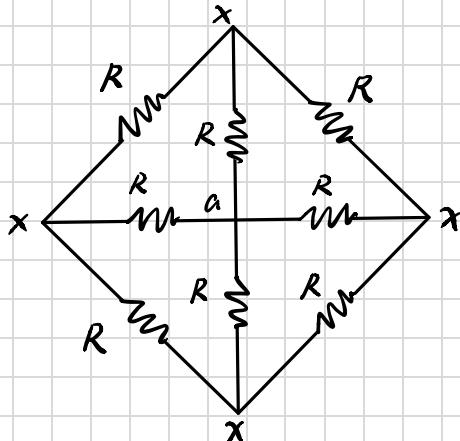3. (a) By the description, the circuit is drawn as follow,



(b) Rewrite the circuit.

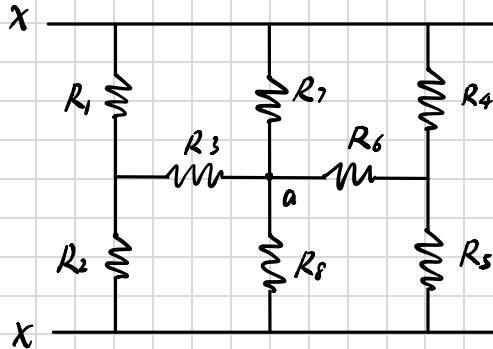


Figure 3.1

Applying $\gamma - \Delta$ conversion,

convert R_1, R_2, R_3 into R_a, R_b, R_c

and R_4, R_5, R_6 into R_d, R_e, R_f

$$R_a = R_b = R_c = R_d = R_e = R_f$$

$$= \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_2} = \frac{3R^2}{R} = 3R$$

Rewrite the circuit as shown in figure 3.2

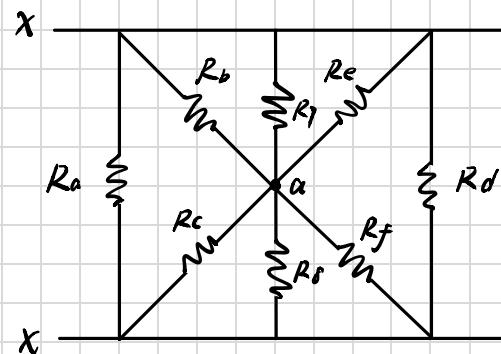


Figure 3.2

Rewrite the circuit as shown in figure 3.3.

$$Req_1 = R_b \parallel R_f \parallel R_e$$

$$= 3R \parallel R \parallel 3R$$

$$= \frac{3}{4}R \parallel 3R$$

$$= \frac{3}{5}R$$

$$Req_2 = Req_1 = \frac{3}{5}R$$

$$Req_3 = R_a \parallel R_d$$

$$= 3R \parallel 3R$$

$$= \frac{3}{2}R$$

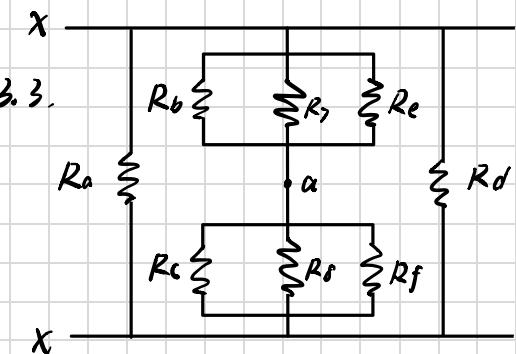


Figure 3.3

Therefore, the total resistance
of a-x pairs is

$$R_{T1} = Req_1 \parallel (Req_2 + Req_3)$$

$$= \frac{3}{5}R \parallel \frac{21}{10}R$$

$$= \frac{7}{15}R$$

#

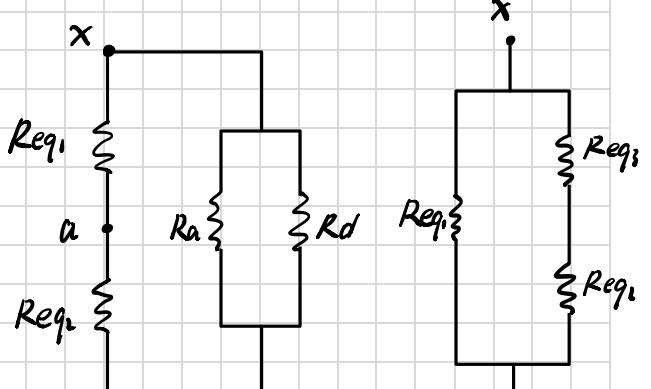


Figure 3.4

Figure 3.5

(C) Rewrite the circuit,

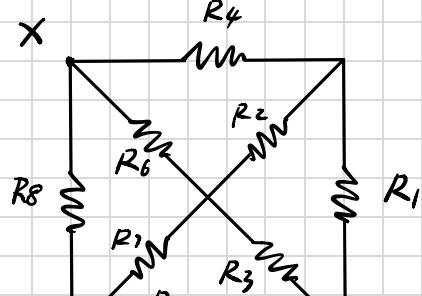


Figure 3.6

Apply $\Delta - Y$ conversion.

convert R_1, R_2, R_3 into R_a, R_b, R_c

$$R_a = R_b = R_c = \frac{R_1 R_2}{R_1 + R_2 + R_3} = \frac{R^2}{3R} = \frac{R}{3}$$

Rewrite the circuit as figure 3.7 shows.

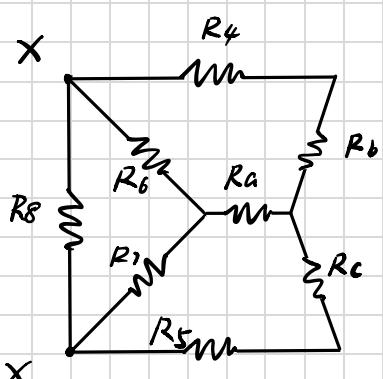


Figure 3.7

$$R_d = R_4 + R_5 = R + \frac{R}{3} = \frac{4}{3}R$$

$$R_e = R_5 + R_c = R + \frac{R}{3} = \frac{4}{3}R$$

Rewrite the circuit, we have
figure 3.8

Apply $\Delta - Y$ conversion.

convert R_d, R_6, R_a into R_o, R_p, R_q

$$R_o = \frac{R_d R_6}{R_d + R_6 + R_a} = \frac{\frac{4}{3}R \cdot R}{\frac{4}{3}R + R + \frac{R}{3}} = \frac{1}{2}R$$

$$R_p = \frac{R_d R_a}{R_d + R_6 + R_a} = \frac{\frac{4}{3}R \cdot \frac{1}{3}R}{\frac{4}{3}R + R + \frac{R}{3}} = \frac{1}{6}R$$

$$R_q = \frac{R_a R_6}{R_d + R_6 + R_a} = \frac{\frac{1}{3}R \cdot R}{\frac{4}{3}R + R + \frac{R}{3}} = \frac{1}{8}R$$

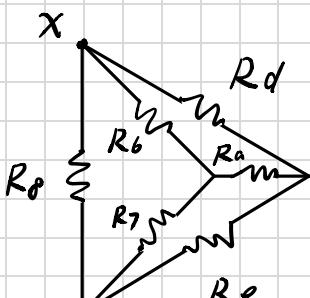


Figure 3.8

Rewrite the circuit as figure 3.9 shows.

$$R_m = R_7 + R_q = R + \frac{1}{8}R = \frac{9}{8}R$$

$$R_n = R_e + R_p = \frac{4}{3}R + \frac{1}{6}R = \frac{3}{2}R$$

Therefore, the total resistance of $x-x$ pairs is

$$\begin{aligned} R_{T_2} &= R_8 \parallel (R_o + R_m \parallel R_n) \\ &= R \parallel (\frac{1}{2}R + \frac{9}{8}R \parallel \frac{3}{2}R) \\ &= \frac{8}{15}R \end{aligned}$$

#

Since $R_{T_1} = \frac{7}{15}R \neq R_{T_2}$, the total resistance is not similar for all possible vertex pairs.



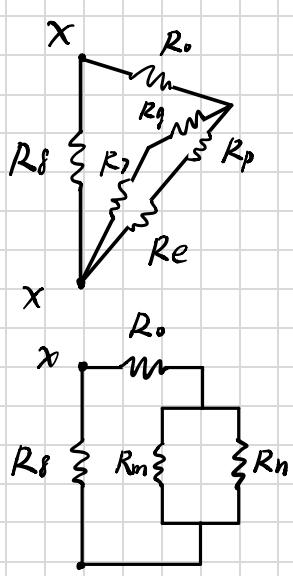


Figure 3.9

4. (a)

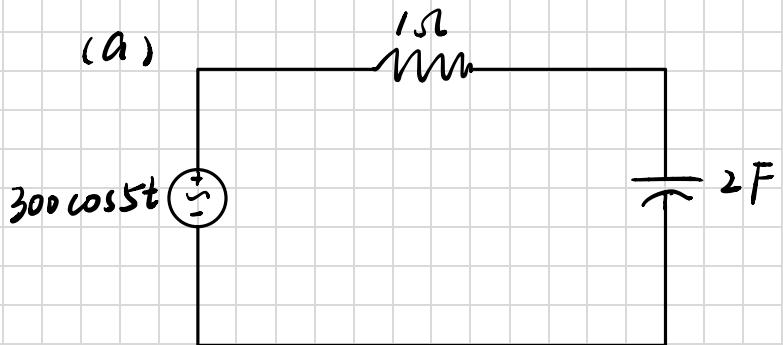

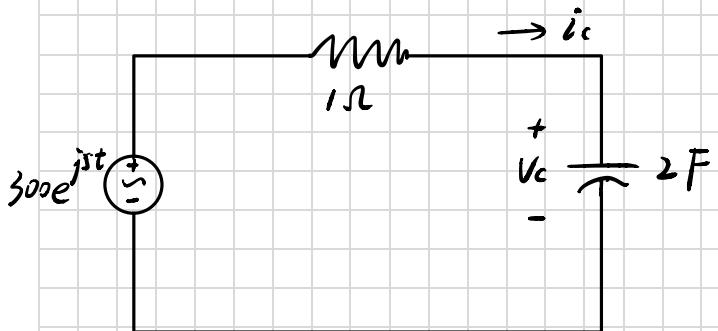(b) Replace the real source with a complex source $300e^{jst} V$, and rewrite the circuit.



Apply KVL to the circuit,

$$-300e^{jst} + 1 \cdot i_c + V_c = 0$$

$$-300e^{jst} + \frac{dV_c}{dt} + V_c = 0$$

We anticipate a steady-state response of the same form as source, what means.

$$V_c = V_m e^{jst}$$

$$\text{Therefore } -300e^{jst} + \frac{d(V_m e^{jst})}{dt} + V_m e^{jst} = 0$$


$$-300e^{jst} + j10V_m e^{jst} + V_m e^{jst} = 0$$

$$V_m = \frac{300}{1+j10} = \frac{300}{\sqrt{1+10^2}} / \tan^{-1}\left(\frac{10}{1}\right) = 29.85 e^{-j84.3^\circ}$$

The steady-state capacitor voltage is

$$\text{Re}\{V_c\} = \text{Re}\{29.85 e^{-j84.3^\circ} e^{jst} V\} = 29.85 \cos(5t - 84.3^\circ) V$$

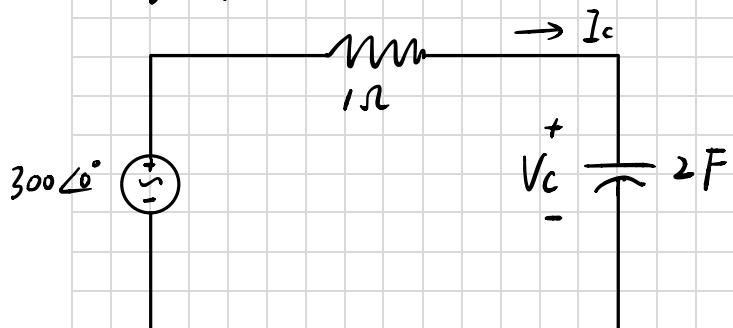(c) Replace the real source with a complex source in frequency-domain $300 \angle 0^\circ V$, and rewrite the circuit.



Apply KVL to the circuit,

$$-300 \angle 0^\circ + 1 \cdot i_c + V_c = 0$$

Since in frequency-domain, the voltage-current express is

$$V = \frac{1}{j\omega C} I \quad \text{the equation is}$$

$$-300 \angle 0^\circ + 1 \cdot I_C + \frac{1}{j\omega C} I_C = 0$$

$$I_C = \frac{300 \angle 0^\circ}{1 + \frac{1}{j\omega C}} = \frac{300 \angle 0^\circ}{1 + \frac{1}{j10}}$$

$$\text{Since in frequency-domain, } Z_C = \frac{1}{j\omega C} = \frac{1}{j10} \Omega,$$

$$V_C = I_C \cdot Z_C$$

$$= \frac{300 \angle 0^\circ}{1 + \frac{1}{j10}} \cdot \frac{1}{j10}$$

$$= \frac{1}{j10 + 1} \cdot 300 \angle 0^\circ$$

$$= \frac{300}{j10 + 1} \cdot \angle 0^\circ$$

$$= 29.85 \angle -84.3^\circ \cdot \angle 0^\circ$$


$$= 29.85 \angle -84.3^\circ$$

#

Therefore the steady-state capacitor voltage is $29.85 \cos(5t - 84.3^\circ)$

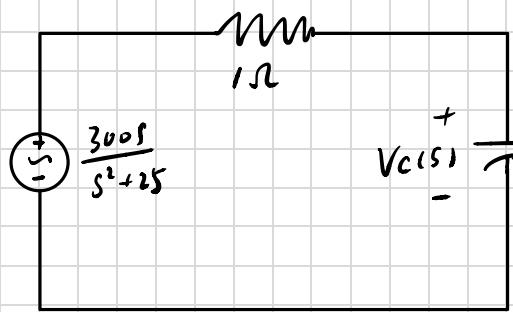(d) Replace the real source with a complex source in s-domain $\frac{300s}{s^2 + 25}$ V. and rewrite the circuit.

By Laplace transform, $Z_C(s) = \frac{1}{sC} = \frac{1}{2s}$



$$I(s) = \frac{V(s)}{1 + Z_C(s)} = \frac{\frac{300s}{s^2 + 25}}{1 + \frac{1}{2s}}$$

$$V_C(s) = I(s) \cdot Z_C(s)$$

$$= \frac{300s}{s^2 + 25} \cdot \frac{\frac{1}{25}}{1 + \frac{1}{25}}$$

$$= \frac{150s}{(s^2 + 25)(s + \frac{1}{2})}$$

$$= \frac{300}{101} \left(\frac{s+50}{s^2+25} - \frac{1}{s+\frac{1}{2}} \right)$$

$$= \frac{300}{101} \frac{s}{s^2+25} + \frac{3000}{101} \frac{5}{s^2+25} - \frac{300}{101} \frac{1}{s+\frac{1}{2}}$$

Since $\cos \omega t u(t) \Rightarrow \frac{s}{s^2 + \omega^2}$

$$\sin \omega t u(t) \Rightarrow \frac{\omega}{s^2 + \omega^2}$$

$$e^{-\alpha t} u(t) \Rightarrow \frac{1}{s+\alpha}$$

By the Linearity theorem and the Homogeneity property.

$$V_C(t) = \mathcal{L}^{-1}\{V_C(s)\}$$

$$= \mathcal{L}^{-1} \left\{ \frac{300}{101} \frac{s}{s^2+25} + \frac{3000}{101} \frac{5}{s^2+25} - \frac{300}{101} \frac{1}{s+\frac{1}{2}} \right\}$$

$$= \frac{300}{101} \mathcal{L}^{-1}\left\{\frac{s}{s^2+25}\right\} + \frac{3000}{101} \mathcal{L}^{-1}\left\{\frac{5}{s^2+25}\right\} - \frac{300}{101} \mathcal{L}^{-1}\left\{\frac{1}{s+\frac{1}{2}}\right\}$$

$$= \frac{300}{101} \cos 5t u(t) + \frac{3000}{101} \sin 5t u(t) - \frac{300}{101} e^{-\frac{1}{2}t} u(t)$$

$$= \frac{300}{\sqrt{101}} \left(\frac{1}{\sqrt{101}} \cos 5t + \frac{10}{\sqrt{101}} \sin 5t \right) u(t) - \frac{300}{101} e^{-\frac{1}{2}t} u(t)$$

$$= \frac{300}{\sqrt{101}} \cos [5t - \tan^{-1}(10)] u(t) - \frac{300}{101} e^{-\frac{1}{2}t} u(t) \quad \#$$

Therefore the steady-state capacitor voltage is $29.85 \cos(5t - 84.3^\circ)$

